

## Chapter 2

# Boolean Arithmetic

These slides support chapter 2 of the book


*The Elements of Computing Systems*

(1<sup>st</sup> and 2<sup>nd</sup> editions)


By Noam Nisan and Shimon Schocken

MIT Press

# Nand to Tetris Roadmap: Hardware

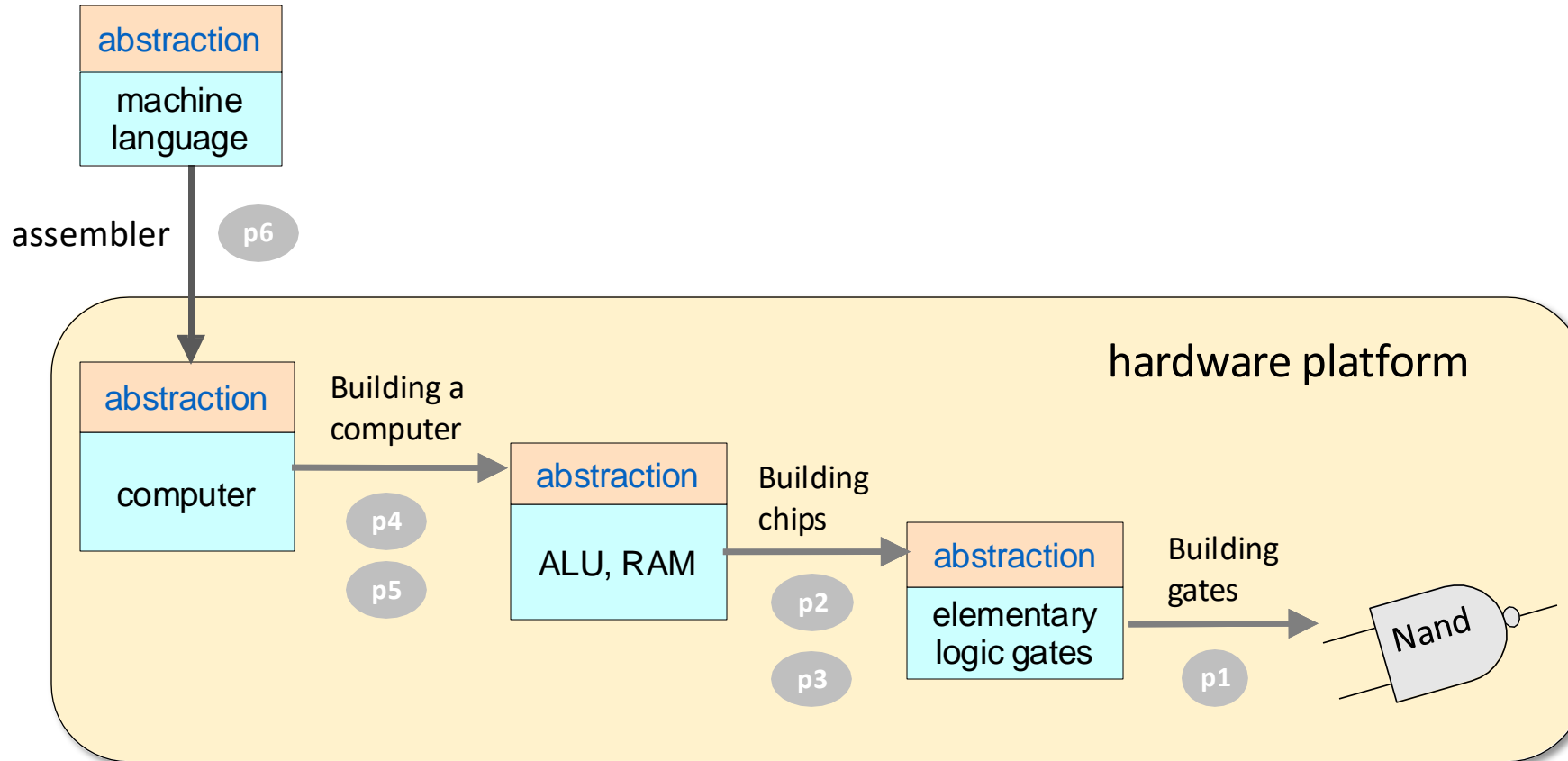


# Nand to Tetris Roadmap: Hardware

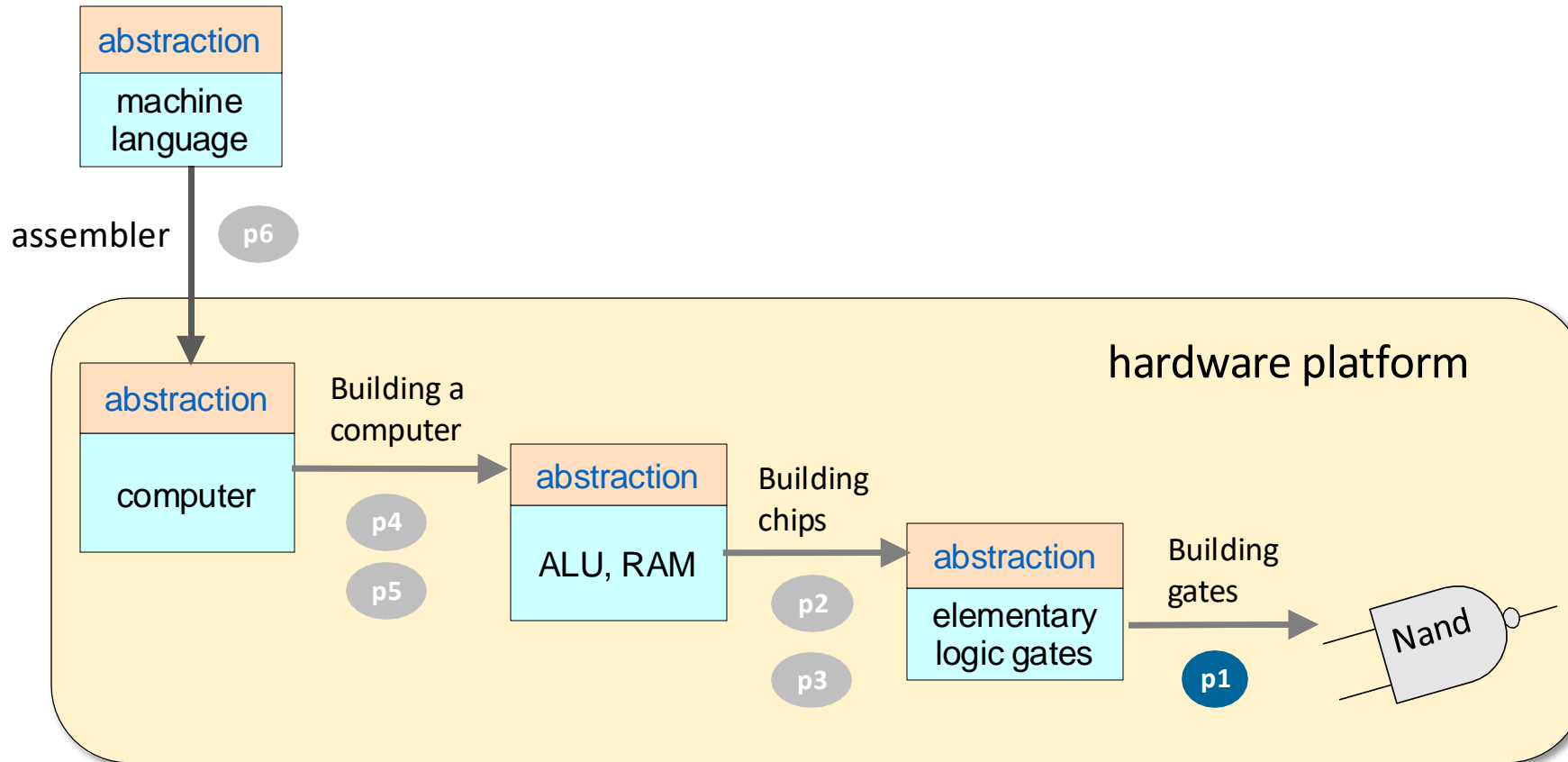

## Project 1

Build 15 elementary logic gates

# Nand to Tetris Roadmap: Hardware

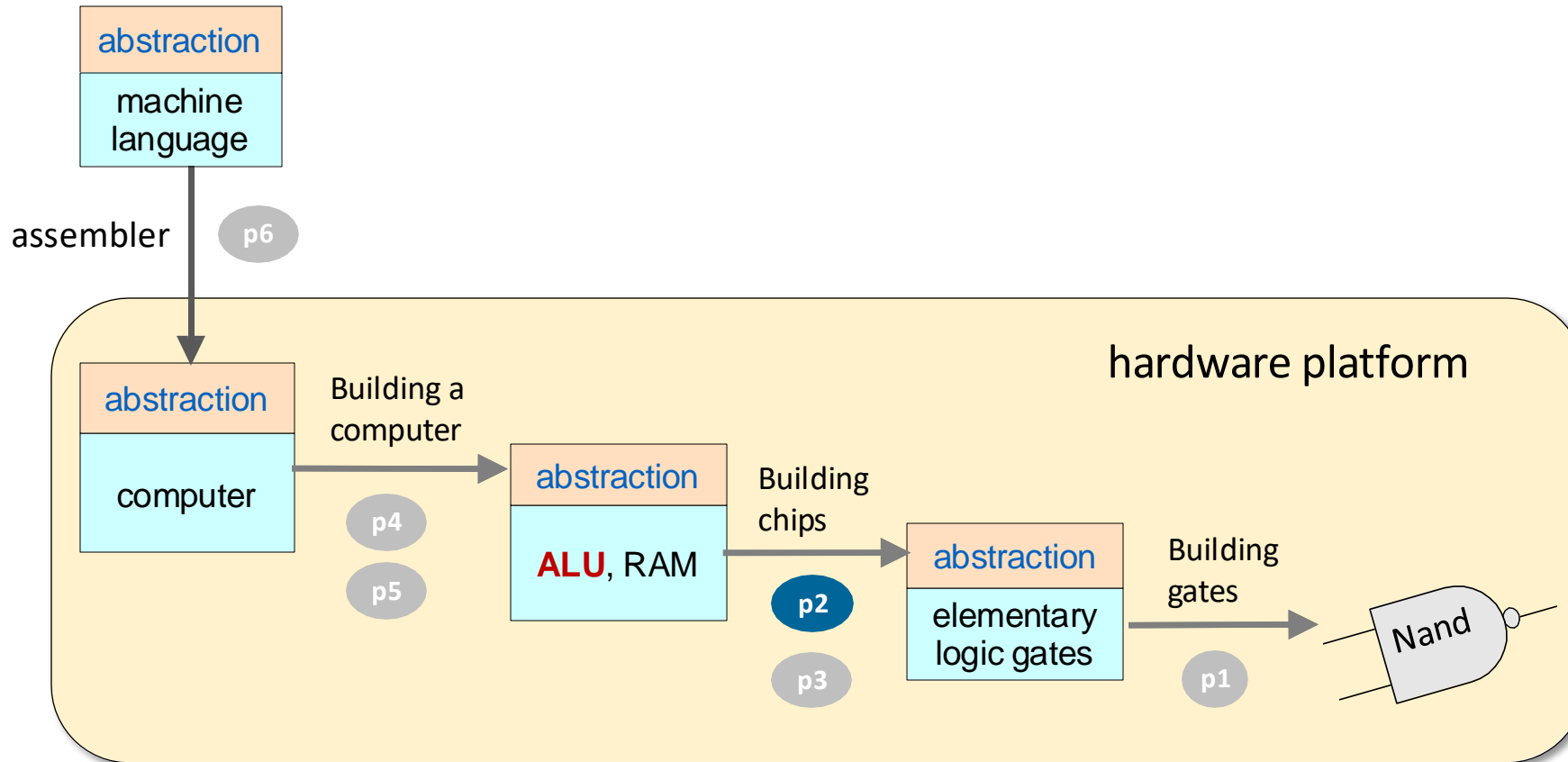


## Project 2

Building chips that do arithmetic,  
ending up with an ALU


# Computer system

---

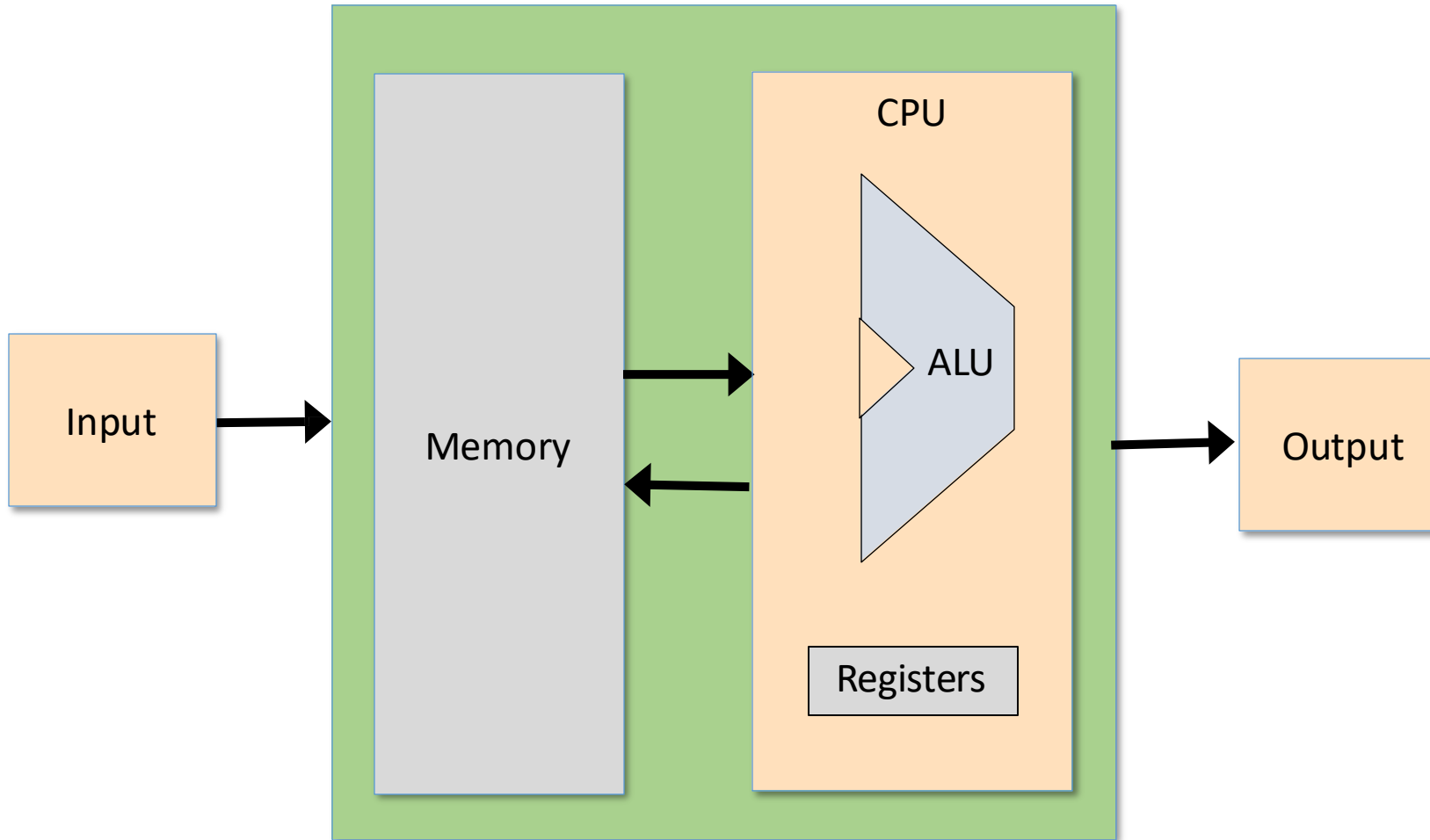


# Computer system

---

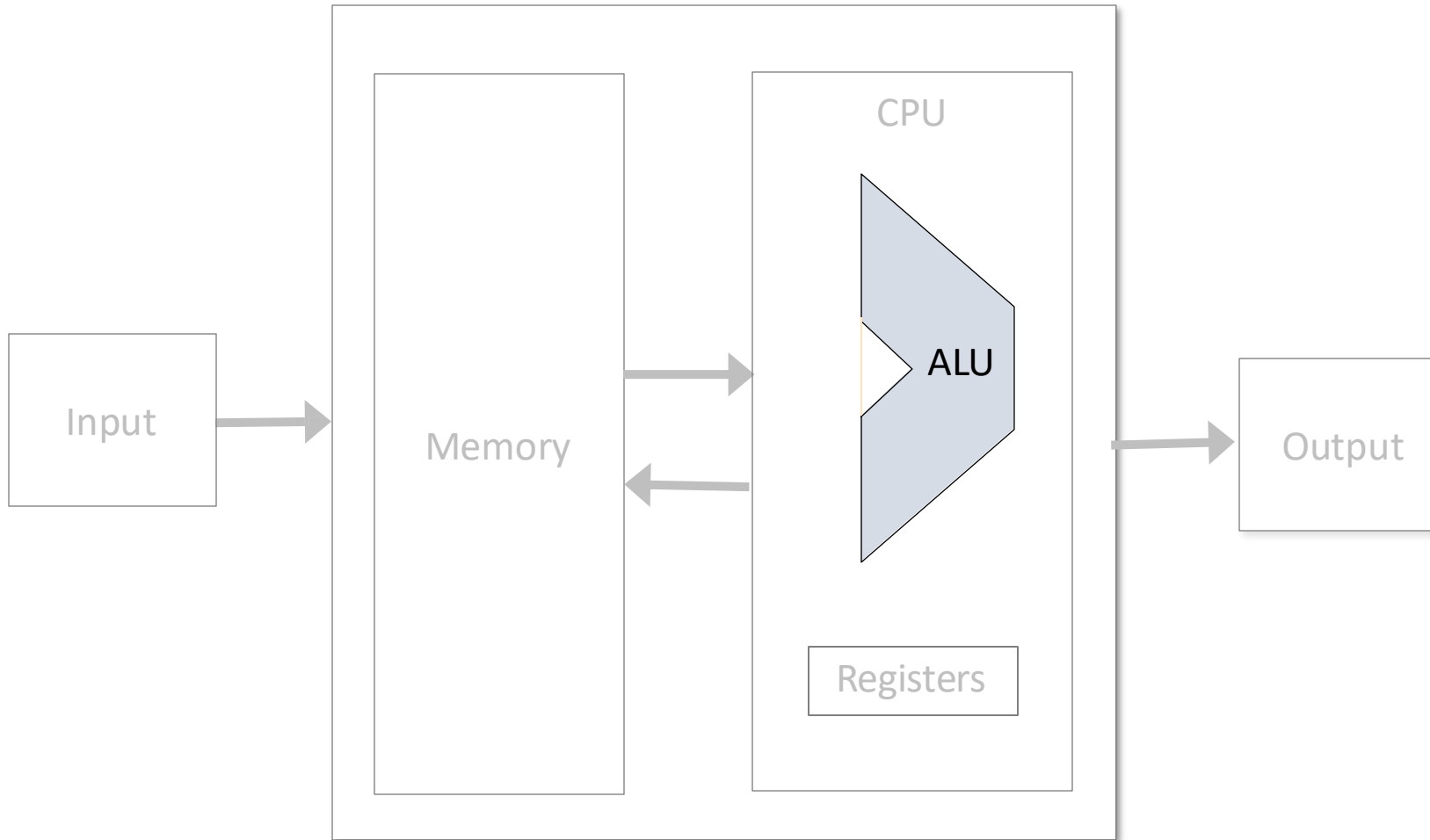

# Arithmetic Logical Unit

---

 

The ALU computes a given function on two given  $n$ -bit values, and outputs an  $n$ -bit value

## ALU functions ( $f$ )

- Arithmetic:  $x + y, x - y, x + 1, x - 1, \dots$
- Logical:  $x \& y, x | y, !x, \dots$

## Challenges

- Use 0's and 1's for representing numbers
- Use logic gates for realizing arithmetic functions.

# Chapter 2: Boolean Arithmetic

---

## Theory

- Representing numbers
- Binary numbers
- Boolean arithmetic
- Signed numbers

## Practice

- Arithmetic Logic Unit (ALU)
- Project 2: Chips
- Project 2: Guidelines



# Chapter 2: Boolean Arithmetic

---

## Theory

### Representing numbers

- Binary numbers
- Boolean arithmetic
- Signed numbers

## Practice

- Arithmetic Logic Unit (ALU)
- Project 2: Chips
- Project 2: Guidelines

# Representation


---



*This is not a pipe*  
(by René Magritte)

# Representation


---

 

Rather, it's an agreed-upon code (*numeral*)  
that represents the number seventeen.

# A brief history of numeral systems

---

 

Twenty seven  
goats

Unary:



Egyptian:




Roman:

XXVII

# A brief history of numeral systems

---

 

Six thousands,  
five hundreds,  
and seven goats

Unary:



Egyptian:




Roman:

MMMMMDVII

## Old numeral systems:

- Don't scale
- Cumbersome arithmetic
- Used until about 1000 years ago
- Blocked the progress of Algebra (and commerce, science, technology)

# Positional numeral system

 

Six thousands,  
five hundreds,  
and seven goats

3 2 1 0  
6 5 0 7

$n \# \$$

!  
 $10^i$   
0

$$d_i \# = 6 \# 10^3 + 5 \# 10^2 + 0 \# 10^1 + 7 \# 10^0 = 6507$$

Where  $n$  is the  
number of  
digits in the  
numeral, and  $d_i$   
is the digit in  
position  $i$

## Positional representation

- *Digits*: A fixed set of symbols, including 0
- *Base*: The number of symbols
- *Numeral*: An ordered sequence of digits
- *Value*: The digit in position  $i$  (counting from right to left, and starting at 0) encodes how many copies of  $base^i$  are added to the value.

A most important innovation, brought  
to the West from the East around 1200

The method mentions  
no specific base.

# Chapter 2: Boolean Arithmetic

---

## Theory



Representing numbers




Binary numbers

- Boolean arithmetic
- Representing signed numbers

## Practice

- Arithmetic Logic Unit (ALU)
- Project 2: Chips
- Project 2: Guidelines

# Positional number system

 

Seven thousands  
and fifty three  
goats

3 2 1 0  
7 0 5 3<sub>10</sub>


$n \# \$$

!  
 $10^i$   
0

$$d_i \# = 7 \# 10^3 + 0 \# 10^2 + 5 \# 10^1 + 3 \# 10^0 = 7053$$



# Positional number system

 

Seven thousands  
and fifty three  
goats

Decimal (base 10) system:  
Human friendly

3 2 1 0  
7 0 5 3<sub>10</sub>

$n \# \$$

$$\begin{matrix} ! \\ 10^i \\ 0 \end{matrix} \quad d_i \# = 7 \# 10^3 + 0 \# 10^2 + 5 \# 10^1 + 3 \# 10^0 = 7053$$

Binary (base 2) system:  
Computer friendly

12 11 10      ...      3 2 1 0  
1 1 0 1 1 0 0 0 1 1 0 1<sub>2</sub>

$n \# \$$

$$\begin{matrix} ! \\ 2^i \\ 0 \end{matrix} \quad d_i \# = 1 \# 2^{12} + 1 \# 2^{11} + 0 \# 2^{10} + \dots + 1 \# 2^0 = 7053$$

# Binary and decimal systems

---

<u>Binary</u>	<u>Decimal</u>
0	0
1	1
1 0	2
1 1	3
1 0 0	4
1 0 1	5
1 1 0	6
1 1 1	7
1 0 0 0	8
1 0 0 1	9
1 0 1 0	10
1 0 1 1	11
1 1 0 0	12
1 1 0 1	13
...	...

Humans are used to enter and view numbers in base 10;

Computers represent and process numbers in base 2;

Therefore, we need efficient algorithms for converting from one base to the other.

# Decimal ↔ binary conversions

---

Powers of 2: (aids in calculations)

$$2^0 = 1$$

$$2^1 = 2$$

$$2^2 = 4$$

$$2^3 = 8$$

$$2^4 = 16$$

$$2^5 = 32$$

$$2^6 = 64$$

$$2^7 = 128$$

$$2^8 = 256$$

$$2^9 = 512$$

$$2^{10} = 1024$$

...

Binary to decimal:

$$\text{decimal } (\overset{5}{1}\overset{4}{1}\overset{3}{0}\overset{2}{1}\overset{1}{0}\overset{0}{1}_2) = 2^5 + 2^4 + 2^2 + 2^0 = 53_{10}$$

Decimal to binary:

$$\text{binary } (53_{10}) = 2^5 + 2^4 + 2^2 + 2^0 = \overset{5}{1}\overset{4}{1}\overset{3}{0}\overset{2}{1}\overset{1}{0}\overset{0}{1}_2$$

Algorithm: What is the largest power of 2 that “fits into” 53? It’s  $32 = 2^5$ . We still have to handle  $53 - 32$ , so, what is the largest power of 2 that fits into 21? It’s  $16 = 2^4$ , and so on.

Practice:

$$\text{decimal } (1011010_2) = ?$$

$$\text{binary } (523_{10}) = ?$$

# Decimal ↔ binary conversions

---

Powers of 2: (aids in calculations)

$$2^0 = 1$$

$$2^1 = 2$$

$$2^2 = 4$$

$$2^3 = 8$$

$$2^4 = 16$$

$$2^5 = 32$$

$$2^6 = 64$$

$$2^7 = 128$$

$$2^8 = 256$$

$$2^9 = 512$$

$$2^{10} = 1024$$

...

Binary to decimal:

$$\text{decimal } (\overset{5}{1}\overset{4}{1}\overset{3}{0}\overset{2}{1}\overset{1}{0}\overset{0}{1}_2) = 2^5 + 2^4 + 2^2 + 2^0 = 53_{10}$$

Decimal to binary:

$$\text{binary } (53_{10}) = 2^5 + 2^4 + 2^2 + 2^0 = \overset{5}{1}\overset{4}{1}\overset{3}{0}\overset{2}{1}\overset{1}{0}\overset{0}{1}_2$$

Algorithm: What is the largest power of 2 that “fits into” 53? It’s  $32 = 2^5$ . We still have to handle  $53 - 32$ , so, what is the largest power of 2 that fits into 21? It’s  $16 = 2^4$ , and so on.

Practice:

$$\text{decimal } (1011010_2) = 90_{10}$$


$$\text{binary } (523_{10}) = 1000001011_2$$

# The binary system



G.W. Leibnitz  
(1646 – 1716)

Worshipped  
binary numbers

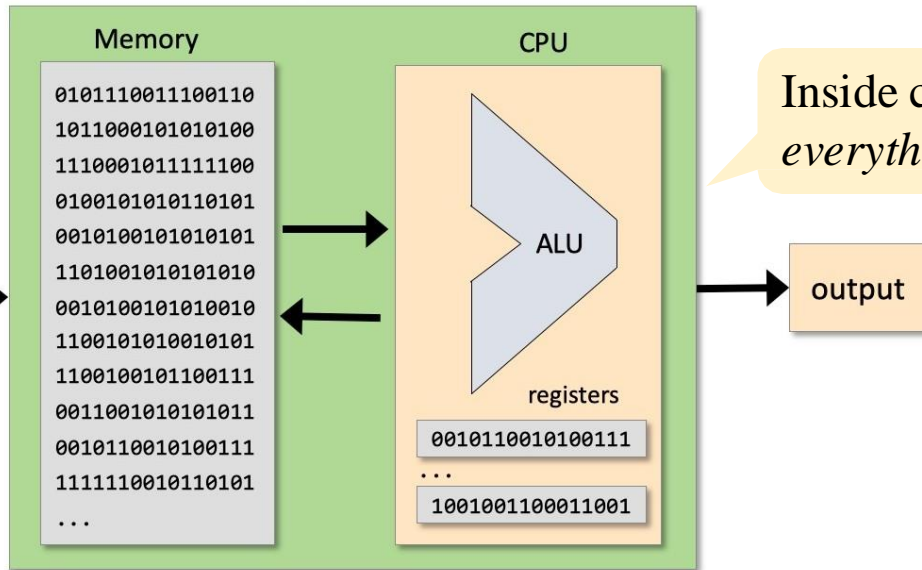

Inside computers,  
*everything* is binary

Binary numerals are easy to:

- Compare
- Add
- Subtract
- Multiply
- Divide
- ...
- Store
- Transmit
- Verify
- Correct
- Compress
- ...



# Chapter 2: Boolean Arithmetic

---

## Theory

✓ Representing numbers

✓ Binary numbers

➡ Boolean arithmetic

- Signed numbers

## Practice

- Arithmetic Logic Unit (ALU)




- Project 2: Chips

- Project 2: Guidelines

# Boolean arithmetic

---

We have to figure out efficient ways to perform, *on binary numbers*:

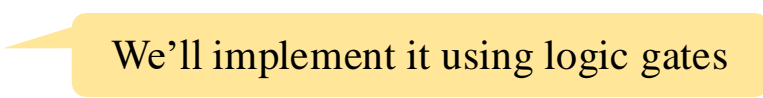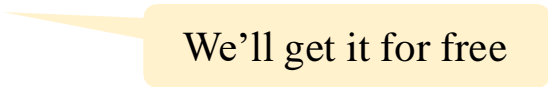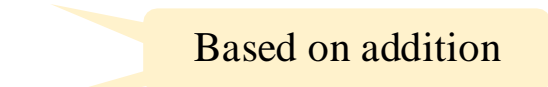- ➔ Addition  We'll implement it using logic gates
- Subtraction  We'll get it for free
- Multiplication  Based on addition
- Division

*Addition* is the foundation of all arithmetic operations.

# Addition

---

$$\begin{array}{rcccc} 0 & 0 & 1 & 0 \\ + & 1 & 0 & 1 & 0 \\ & & & 1 & 1 \\ \hline 1 & 1 & 0 & 1 \end{array}$$

Binary addition

$$\begin{array}{rcccc} 0 & 1 & 1 & 0 \\ + & 7 & 8 & 7 & 5 \\ & & 5 & 6 & 2 \\ \hline 8 & 4 & 3 & 7 \end{array}$$

Decimal addition



# Addition

---

Computers represent integers using a fixed number of bits, sometimes called “word size”. For example, let’s assume  $n = 4$ :

$$\begin{array}{r} 0 \ 0 \ 1 \ 0 \\ + \begin{array}{|c|c|c|c|} \hline 1 & 0 & 1 & 0 \\ \hline 0 & 0 & 1 & 1 \\ \hline \end{array} \\ \hline \begin{array}{|c|c|c|c|} \hline 1 & 1 & 0 & 1 \\ \hline \end{array} \end{array}$$

Binary addition

$$\begin{array}{r} 0 \ 0 \ 1 \\ + \begin{array}{|c|c|c|c|} \hline 0 & 0 & 0 & 1 \\ \hline 0 & 1 & 0 & 1 \\ \hline \end{array} \\ \hline \begin{array}{|c|c|c|c|} \hline 0 & 1 & 1 & 0 \\ \hline \end{array} \end{array}$$

Another example

$$\begin{array}{r} \textcolor{red}{1} \ 1 \ 1 \ 0 \\ + \begin{array}{|c|c|c|c|} \hline 0 & 1 & 1 & 1 \\ \hline 1 & 1 & 1 & 0 \\ \hline \end{array} \\ \hline \textcolor{red}{1} \begin{array}{|c|c|c|c|} \hline 0 & 1 & 0 & 1 \\ \hline \end{array} \end{array}$$

Overflow

## Handling overflow

- Our decision: Ignore it
- As we will soon see, ignoring the overflow bit is not a bug, it’s a feature.

# Addition

Word size  $n = 16, 32, 64, \dots$

$$\begin{array}{cccccccccccccccc} & 0 & \dots & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & 1 & 1 & 1 & 0 & 0 & 0 \\ + & \boxed{0} & \dots & \boxed{0} & \boxed{0} & & \boxed{0} & \boxed{0} & \boxed{0} & \boxed{1} & \boxed{1} & \boxed{0} & \boxed{1} & & \boxed{1} & \boxed{0} & \boxed{1} \\ & \boxed{0} & \dots & \boxed{0} & \boxed{0} & & \boxed{0} & \boxed{0} & \boxed{0} & \boxed{0} & \boxed{1} & \boxed{0} & \boxed{1} & & \boxed{1} & \boxed{0} & \boxed{0} \\ \hline & \boxed{0} & \dots & \boxed{0} & \boxed{0} & & \boxed{0} & \boxed{0} & \boxed{1} & \boxed{0} & \boxed{0} & \boxed{1} & \boxed{1} & & \boxed{0} & \boxed{0} & \boxed{1} \end{array}$$

Same  
addition  
algorithm  
for any  $n$

## Hardware implementation

We'll build an *Adder* chip that implements this addition algorithm,

Using the chips built in project 1.

How? Later.

## Teaching Note

In Nand to Tetris we always separate *abstraction* from *implementation*

First we present the abstraction, leaving the implementation to a later stage in the lecture.

# Chapter 2: Boolean Arithmetic

---

## Theory

- ✓ Representing numbers
- ✓ Binary numbers
- ✓ Boolean arithmetic (addition)
- ➔ • Signed numbers  
 $(x + y, -x + y, x + -y, -x + -y)$

## Practice

- Arithmetic Logic Unit (ALU)
- Project 2: Chips
- Project 2: Guidelines

# Signed integers

---

- Positive
- 0
- Negative

In most programming languages, the short, int, and long data types use 16, 32, and 64 bits for representing signed integers

Arithmetic operations on signed integers ( $x \text{ op } y$ ,  $-x \text{ op } y$ ,  $x \text{ op } -y$ ,  $-x \text{ op } -y$ , where  $\text{op} = \{+, -, *, /\}$ ) are by far what computers do most of the time

Therefore ...

Efficient algorithms for handling arithmetic operations on signed integers hold the key to building efficient computers.

Teaching Note: All the algorithms presented in this course can be implemented efficiently in either hardware or software.

# Signed integers

---

code( $x$ )	$x$
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	10
1011	11
1100	12
1101	13
1110	14
1111	15

This particular example: word size is  $n = 4$

In general,  $n$  bits allow representing all the unsigned integers  $0 \dots 2^n - 1$

What about negative numbers?

We can use half of the code space for representing positive numbers, and the other half for negatives.

# Signed integers

code(x)	x
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	10
1011	11
1100	12
1101	13
1110	14
1111	15

## Representation:

Left-most bit (MSB): Represents the sign, +/-

Remaining bits: Represent a positive integer

## Issues

- $-0$ : Huh?
- $code(x) + code(-x) \neq code(0)$
- The codes are not monotonically increasing
- more complications.

# Two's complement

---

code( $x$ )	$x$
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

## The representation

- Assumption: Word size =  $n$  bits
- The “two’s complement” of  $x$  is defined to be  $2^n - x$
- The negative of  $x$  is coded by the two’s complement of  $x$

## From decimal to binary:

if  $x \geq 0$  return  $binary(x)$   
else return  $binary(2^n - x)$

## From binary to decimal:

if MSB = 0 return  $decimal(bits)$   
else return “-” and then  $(2^n - decimal(bits))$

# Two's complement: Addition

code(x)	x		Compute $x + y$ where $x$ and $y$ are signed	
0000	0	0	Algorithm: Regular addition, modulo $2^n$	
0001	1	1		
0010	2	2		
0011	3	3		
0100	4	4		
0101	5	5		
0110	6	6		
0111	7	7		
1000	8	-8		
1001	9	-7		
1010	10	-6		
1011	11	-5		
1100	12	-4		
1101	13	-3		
1110	14	-2		
1111	15	-1		

$$\begin{array}{rcl}
 + 6 & = & + 6 \\
 -2 & & 14 \\
 \hline
 & & 20 \% 16 = 4 \text{ codes } 4
 \end{array}$$

$$\begin{array}{rcl}
 + 3 & = & + 3 \\
 -5 & & 11 \\
 \hline
 & & 14 \% 16 = 14 \text{ codes } -2
 \end{array}$$

$$\begin{array}{rcl}
 + -2 & = & + 14 \\
 -5 & & 11 \\
 \hline
 & & 25 \% 16 = 9 \text{ codes } -7
 \end{array}$$



# Two's complement: Addition

code(x)	x		Compute $x + y$ where $x$ and $y$ are signed
0000	0	0	Algorithm: Regular addition, modulo $2^n$
0001	1	1	
0010	2	2	
0011	3	3	$\begin{array}{r} + 6 \\ -2 \end{array} = \begin{array}{r} + 6 \\ 14 \end{array}$
0100	4	4	$\frac{14}{20 \% 16 = 4} \text{ codes } 4$
0101	5	5	
0110	6	6	Practice:
0111	7	7	
1000	8	-8	
1001	9	-7	$\begin{array}{r} + 4 \\ -7 \end{array} = ?$
1010	10	-6	
1011	11	-5	
1100	12	-4	
1101	13	-3	$\begin{array}{r} -2 \\ + -4 \end{array} = ?$
1110	14	-2	
1111	15	-1	

# Two's complement: Addition

code(x)	x		Compute $x + y$ where $x$ and $y$ are signed	
0000	0	0	Algorithm: Regular addition, modulo $2^n$	
0001	1	1		
0010	2	2		
0011	3	3		
0100	4	4		
0101	5	5		
0110	6	6		
0111	7	7		
1000	8	-8		
1001	9	-7		
1010	10	-6		
1011	11	-5		
1100	12	-4		
1101	13	-3		
1110	14	-2		
1111	15	-1		

Compute  $x + y$  where  $x$  and  $y$  are signed

Algorithm: Regular addition, modulo  $2^n$

$$\begin{array}{rcl}
 + 6 & = & + 6 \\
 -2 & & 14 \\
 \hline
 20 \% 16 = 4 & \text{codes } 4
 \end{array}$$

Practice:

$$\begin{array}{rcl}
 + 4 & = & + 4 \\
 -7 & & 9 \\
 \hline
 13 \% 16 = 13 & \text{codes } -3
 \end{array}$$

$$\begin{array}{rcl}
 + -2 & = & + 14 \\
 + -4 & & 12 \\
 \hline
 26 \% 16 = 10 & \text{codes } -6
 \end{array}$$

# Two's complement: Addition

code(x)	x	
0000	0	0
0001	1	1
0010	2	2
0011	3	3
0100	4	4
0101	5	5
0110	6	6
0111	7	7
1000	8	-8
1001	9	-7
1010	10	-6
1011	11	-5
1100	12	-4
1101	13	-3
1110	14	-2
1111	15	-1

At the binary level (same algorithm):

$$\begin{array}{rcl}
 +6 & = & +0110 \\
 -2 & & +1110 \\
 \hline
 & & 10100 \text{ codes } 4
 \end{array}$$
  

$$\begin{array}{rcl}
 +3 & = & +0011 \\
 -5 & & +1011 \\
 \hline
 & & 1110 \text{ codes } -2
 \end{array}$$
  

$$\begin{array}{rcl}
 -2 & = & +1110 \\
 +5 & & +1011 \\
 \hline
 & & 11001 \text{ codes } -7
 \end{array}$$

Ignoring the overflow bit  
is the binary equivalent of  
modulo  $2^n$

# Two's complement: Addition

code(x)	x
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	10
1011	11
1100	12
1101	13
1110	14
1111	15

At the binary level (same algorithm):

$$\begin{array}{r}
 \phantom{+} 6 \\
 + \phantom{00} \\
 \hline
 \phantom{+} -2 \\
 + \phantom{00} \\
 \hline
 \phantom{+} 0110 \\
 + \phantom{+} 1110 \\
 \hline
 \phantom{+} 10100
 \end{array}
 \quad \text{codes } 4$$

More examples:

$$\begin{array}{r}
 \phantom{+} 5 \\
 + \phantom{00} \\
 \hline
 \phantom{+} 7 \\
 + \phantom{00} \\
 \hline
 \phantom{+} 0101 \\
 + \phantom{+} 0111 \\
 \hline
 \phantom{+} 1100
 \end{array}
 \quad \text{codes } -4 \quad 5 + 7 = -4 \quad ???$$

$$\begin{array}{r}
 \phantom{+} -7 \\
 + \phantom{00} \\
 \hline
 \phantom{+} -3 \\
 + \phantom{00} \\
 \hline
 \phantom{+} 1001 \\
 + \phantom{+} 1101 \\
 \hline
 \phantom{+} 10110
 \end{array}
 \quad \text{codes } 6 \quad -7 + -3 = 6 \quad ???$$

## Overflow detection

When you add up two positives (negatives) and get a negative (positive) result, you know that you have overflow

# Two's complement: Subtraction

---

code( $x$ )	$x$	<u>Compute <math>x - y</math></u> where $x$ and $y$ are signed
0000	0	0
0001	1	1
0010	2	2
0011	3	3
0100	4	4
0101	5	5
0110	6	6
0111	7	7
1000	8	-8
1001	9	-7
1010	10	-6
1011	11	-5
1100	12	-4
1101	13	-3
1110	14	-2
1111	15	-1

- $x - y$  is the same as  $x + (-y)$
- So... convert  $y$  and add up the two values  
(we already know how to add up signed numbers)

But ... How to convert a number (efficiently)?

# Two's complement: Sign conversion

---

code(x)	x
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	10
1011	11
1100	12
1101	13
1110	14
1111	15

Compute  $-x$  from  $x$

Insight:  $code(-x) = (2^n - x) = 1 + (2^n - 1) - x$   
 $= 1 + (1111) - x$   
 $= 1 + flippedBits(x)$

Algorithm: To convert  $bbb...b$ :

Flip all the bits and add 1 to the result

Example: Convert 0010 (2)

$$\begin{array}{r}
 1101 \text{ (flipped)} \\
 + \quad 1 \\
 \hline
 1110 \text{ (-2)}
 \end{array}$$

# Two's complement: Sign conversion

---

code(x)	x
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

Compute  $-x$  from  $x$

Insight:  $code(-x) = (2^n - x) = 1 + (2^n - 1) - x$   
 $= 1 + (1111) - x$   
 $= 1 + flippedBits(x)$

Algorithm: To convert  $bbb...b$ :

Flip all the bits and add 1 to the result

Practice: Convert 1010 (-6)

# Two's complement: Sign conversion

---

code(x)	x
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	10
1011	11
1100	12
1101	13
1110	14
1111	15

Compute  $-x$  from  $x$

Insight:  $code(-x) = (2^n - x) = 1 + (2^n - 1) - x$   
 $= 1 + (1111) - x$   
 $= 1 + flippedBits(x)$

Algorithm: To convert  $bbb...b$ :

Flip all the bits and add 1 to the result

Practice: Convert 1010 ( $-6$ )

$$\begin{array}{r}
 0101 \text{ (flipped)} \\
 + \quad 1 \\
 \hline
 0110 \text{ (6)}
 \end{array}$$

But... How to compute  $x + 1$  (*efficiently*)?



# Two's complement: Add 1

---

code( $x$ )	$x$	
0000	0	<u>Compute <math>x + 1</math></u> (efficiently)
0001	1	Given $bbb...b$ , compute $bbb...b + 1$
0010	2	
0011	3	<u>Algorithm</u> : Flip bits from right to left,
0100	4	stop when the flipped bit becomes 1
0101	5	
0110	6	<u>Example</u> : Compute $0101 + 1$ ( $5 + 1$ )
0111	7	$0110$ ( $6$ )
1000	8	
1001	9	
1010	10	<u>Practice</u> : Compute $0110 + 1$ ( $6 + 1$ )
1011	11	Compute $0011 + 1$ ( $3 + 1$ )
1100	12	Compute $1000 + 1$ ( $-8 + 1$ )
1101	13	Compute $1011 + 1$ ( $-5 + 1$ )
1110	14	
1111	15	

# Two's complement: Recap

---

code(x)	x	Observations
0000	0	<ul style="list-style-type: none"><li>The method represents all the integers in the range <math>-2^{n-1}, \dots, -1, 0, 1, \dots, 2^{n-1} - 1</math></li><li><math>code(x) + code(-x) = code(0)</math></li><li>The codes are monotonically increasing</li><li>Arithmetic on signed integers is the same as arithmetic on unsigned integers</li><li>Simple! Elegant! Powerful!</li></ul>
0001	1	
0010	2	
0011	3	
0100	4	
0101	5	
0110	6	
0111	7	
1000	8	<u>Implications for hardware designers</u> Arithmetic on signed integers can be implemented using <i>the same hardware</i> used for handling arithmetic of unsigned integers
1001	9	
1010	10	
1011	11	
1100	12	
1101	13	
1110	14	
1111	15	

# Chapter 2: Boolean Arithmetic

---

## Theory

- Representing numbers
- Binary numbers
- Boolean arithmetic
- Signed numbers



## Practice

- Arithmetic Logic Unit (ALU)
- Project 2: Chips
- Project 2: Guidelines

# Chapter 2: Boolean Arithmetic

---

## Theory

- Representing numbers
- Binary numbers
- Boolean arithmetic
- Signed numbers

## Practice




Arithmetic Logic Unit (ALU)

- Project 2: Chips
- Project 2: Guidelines

# Von Neumann Architecture

---

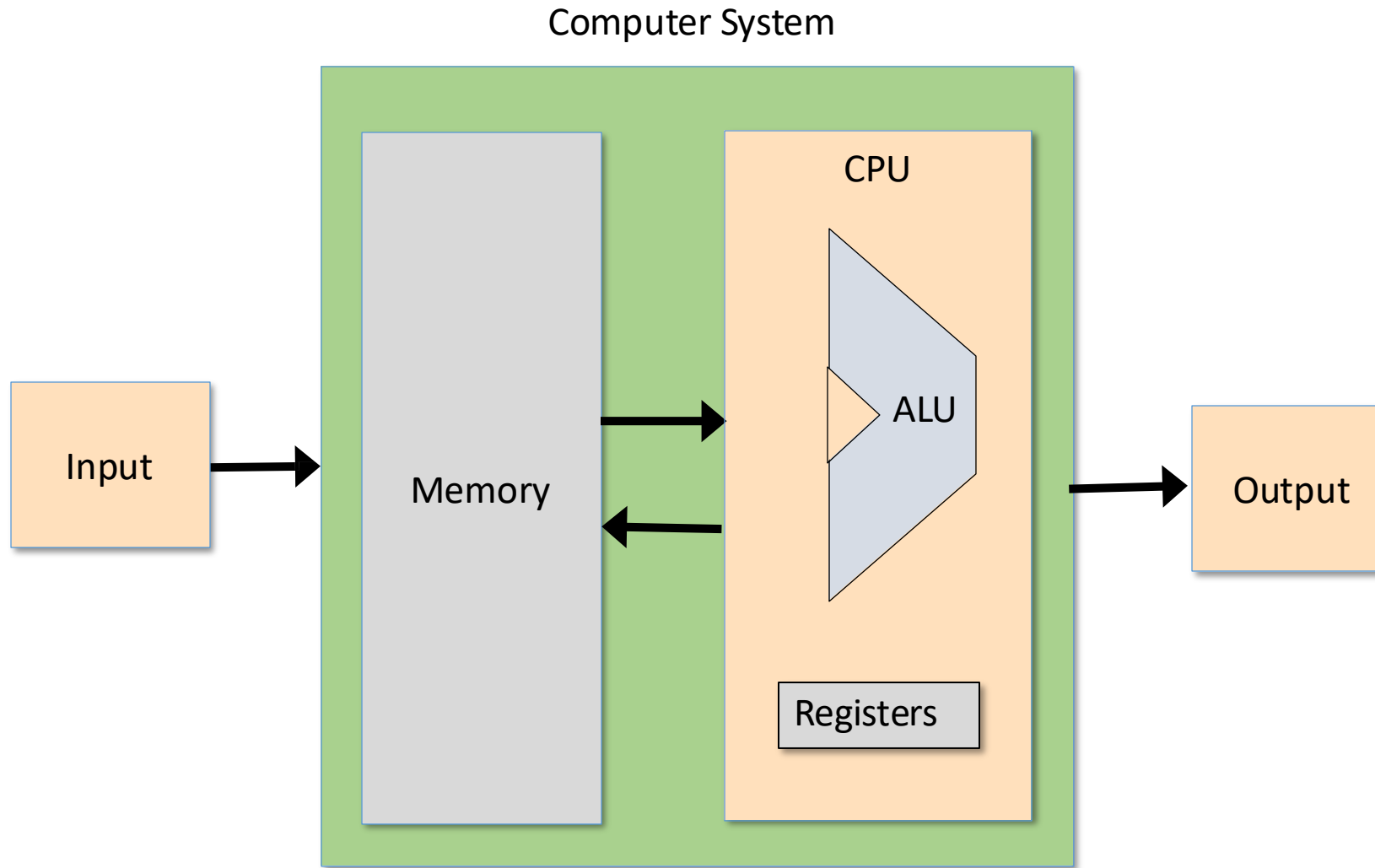


# The Arithmetic Logical Unit

---

The ALU computes a given function on its two given data inputs, and outputs the result

 $f$ : one out of a family of pre-defined arithmetic functions (*add, subtract, multiply...*) and logical functions (*And, Or, Xor, ...*)



Design issue: Which functions should the ALU perform?


A hardware / software tradeoff: Any function not implemented by the ALU can be implemented later in system software

- Hardware implementations: Faster, and more expensive
- Software implementations: Slower, less expensive
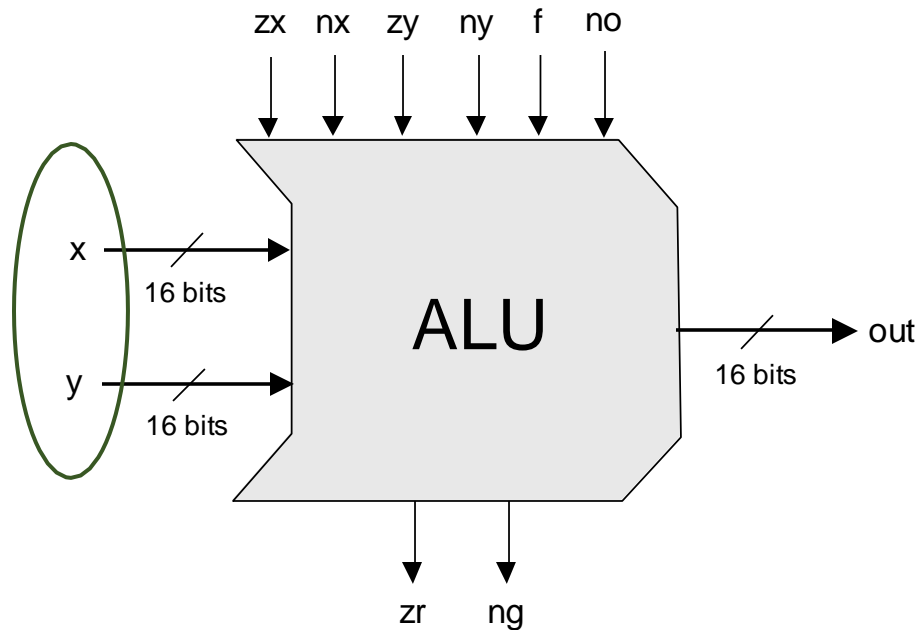
# The Hack ALU


---

- Operates on two 16-bit, two's complement values


 
# The Hack ALU

- Operates on two 16-bit, two's complement values
- Outputs a 16-bit, two's complement value




out

0
1
-1
x
y
!x
!y
-x
-y
x+1
y+1
x-1
y-1
x+y
x-y
y-x
x&y
x y


 
# The Hack ALU

- Operates on two 16-bit, two's complement values
- Outputs a 16-bit, two's complement value
- Also outputs two 1-bit values (later)




out

0
1
-1
x
y
!x
!y
-x
-y
x+1
y+1
x-1
y-1
x+y
x-y
y-x
x&y
x y
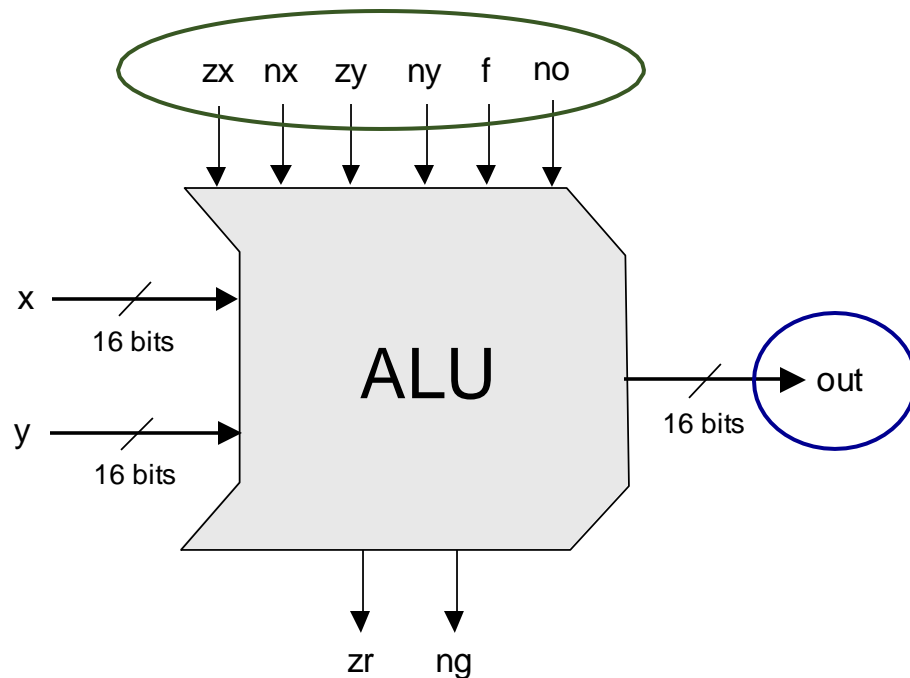
# The Hack ALU

- Operates on two 16-bit, two's complement values
- Outputs a 16-bit, two's complement value
- Also outputs two 1-bit values (later)
- Which function to compute is set by six 1-bit inputs




out

0
1
-1
x
y
!x
!y
-x
-y
x+1
y+1
x-1
y-1
x+y
x-y
y-x
x&y
x y
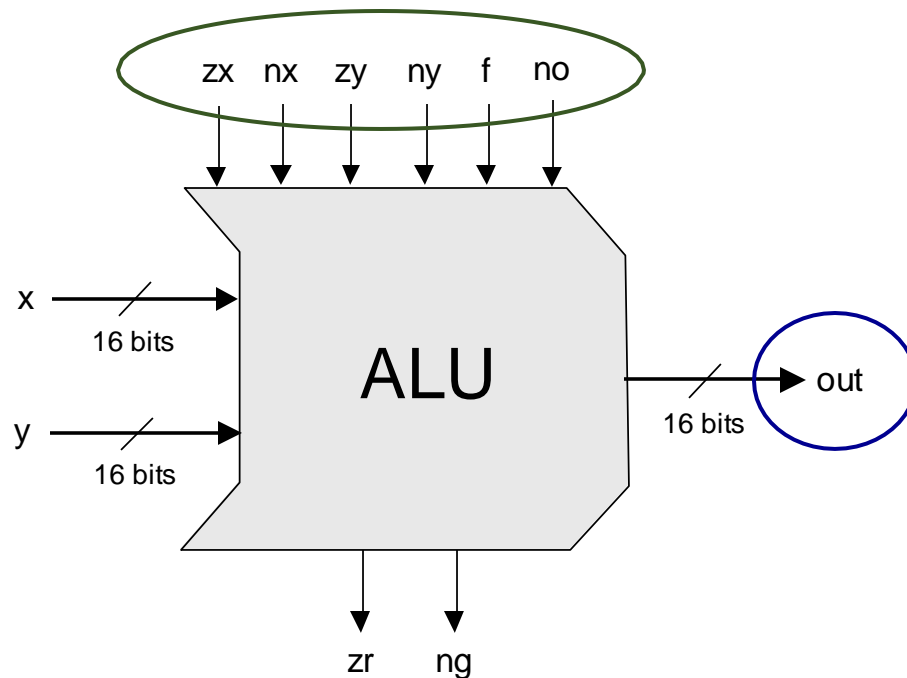
# The Hack ALU

To cause the ALU to compute a function:

Set the control bits to one of the binary combinations listed in the table.




control bits						
zx	nx	zy	ny	f	no	out
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y
 
# The Hack ALU in action: Compute $y-x$

To cause the ALU to compute a function:

Set the control bits to one of the binary combinations listed in the table.



control bits						
$zx$	$nx$	$zy$	$ny$	$f$	$no$	out
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	$x$
1	1	0	0	0	0	$y$
0	0	1	1	0	1	$!x$
1	1	0	0	0	1	$!y$
0	0	1	1	1	1	$-x$
1	1	0	0	1	1	$-y$
0	1	1	1	1	1	$x+1$
1	1	0	1	1	1	$y+1$
0	0	1	1	1	0	$x-1$
1	1	0	0	1	0	$y-1$
0	0	0	0	1	0	$x+y$
0	1	0	0	1	1	$x-y$
0	0	0	1	1	1	$y-x$
0	0	0	0	0	0	$x \& y$
0	1	0	1	0	1	$x   y$

# The Hack ALU in action: Compute $y-x$

The screenshot shows the Nand2Tetris IDE interface. The top toolbar contains icons for running, stepping, and pausing, with the calculator icon circled and labeled "2. Evaluate the chip logic". Below the toolbar, the "Ch Nam..." field is set to "ALU". The "Input" table shows control bits: 

Name	Value
zy	0
ny	1
f	1
no	1

. A callout "Load tools/builtInChips/ALU.hdl" points to the input table. The "Output pins" table shows: 

Name	Value
out[16]	-10
zr	0
ng	1

. A callout "3. Inspect the ALU outputs" points to the output table. The "HDL" editor shows the ALU implementation code. A callout "1. Set the ALU's inputs and control bits to some test values (000111 codes 'output y-x')" points to the control bits. A callout "Built-in ALU implementation" points to the HDL code. The logic diagram at the bottom shows the ALU block with "D Input" 30 and "M/A Input" 20, resulting in "ALU output" -10. A callout "The built-in ALU implementation has GUI side-effects" points to the logic diagram.

2. Evaluate the chip logic

Load tools/builtInChips/ALU.hdl

3. Inspect the ALU outputs

1. Set the ALU's inputs and control bits to some test values (000111 codes "output y-x")

Built-in ALU implementation

The built-in ALU implementation has GUI side-effects

ALU

D Input : 30


M/A Input : 20

ALU output : -10
 
# The Hack ALU in action: Compute $x \& y$

To cause the ALU to compute a function:

Set the control bits to one of the binary combinations listed in the table.



control bits						
$zx$	$nx$	$zy$	$ny$	$f$	$no$	out
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	$x$
1	1	0	0	0	0	$y$
0	0	1	1	0	1	$!x$
1	1	0	0	0	1	$!y$
0	0	1	1	1	1	$-x$
1	1	0	0	1	1	$-y$
0	1	1	1	1	1	$x+1$
1	1	0	1	1	1	$y+1$
0	0	1	1	1	0	$x-1$
1	1	0	0	1	0	$y-1$
0	0	0	0	1	0	$x+y$
0	1	0	0	1	1	$x-y$
0	0	0	1	1	1	$y-x$
0	0	0	0	0	0	$x \& y$
0	1	0	1	0	1	$x   y$

# The Hack ALU in action: Compute $x \& y$

The screenshot shows the Nand2Tetris ALU simulator interface. The top menu bar includes File, View, Run, and Help. Below the menu is a toolbar with icons for running, pausing, and stepping through the simulation, along with speed controls (Slow, Fast) and format/view options (Program flow, Bi..., Scr...). The main window is divided into several sections:


- Chip Name:** ALU, Time: 0
- Input pins:** A table with columns Name and Value. The values for x[16] and y[16] are circled in blue. The control bits zx, nx, zy, ny, f, and no are all set to 0.
- Output pins:** A table with columns Name and Value. The value for out[16] is circled in blue. The zero (zr) and negative (ng) flags are both 0.
- HDL:** A text area containing Verilog code for the ALU. The code is commented to show the logic for computing  $x \& y$  based on the control bits.
- Logic Diagram:** A diagram showing the ALU as a green trapezoid with a 'D&M' block inside. The D Input is -5242 and the M/A Input is 6253. The ALU output is 2052.

Yellow callout boxes provide additional context:

- "Set to binary I/O format" points to the Format dropdown menu.
- "Inspect the ALU outputs" points to the Output pins table.
- "Set the ALU's inputs and control bits to some test values (000000 codes 'compute x&y')" points to the Input pins table.

# The Hack ALU operation

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=

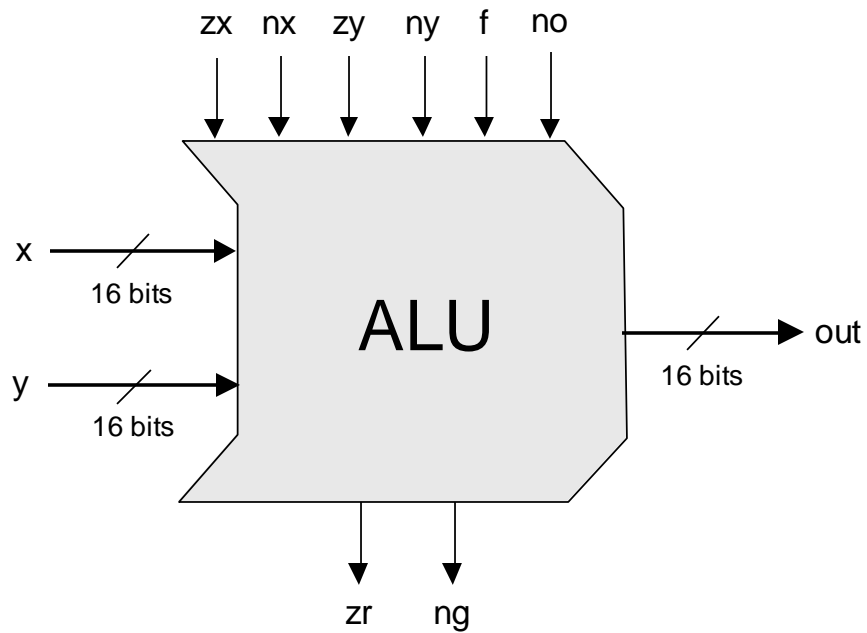



# The Hack ALU operation

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

# The Hack ALU operation: Compute !x

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0					-x
1	1					-y
0	1					x+1
1	1					y+1
0	0					x-1
1	1					y-1
0	0					x+y
0	1					x-y
0	0					y-x
0	0					x&y
0	1					x y

Example: compute !x

x:        1 1 0 0

y:        1 0 1 1 (irrelevant)

Following pre-setting:

x:        1 1 0 0

y:        1 1 1 1

Computation and post-setting:

x&y:      1 1 0 0

!(x&y):   0 0 1 1 (!x)

## The Hack ALU operation: Compute $y-x$

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
<b>zx</b>	<b>nx</b>	<b>zy</b>	<b>ny</b>	<b>f</b>	<b>no</b>	<b>out</b>
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	1
0	0	1	1	1	0	0
1	1	0	0	1	0	x
0	0	1	1	1	0	y
1	1	0	0	1	0	1
0	0	1	1	1	0	x
1	1	0	0	1	0	y
0	0	1	1	1	0	1
1	1	0	0	1	0	1
0	0	1	1	1	0	1
1	1	0	0	1	0	1
0	0	0	0	0	0	y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

# The Hack ALU operation: Compute $x|y$

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1					-1
0	0					x
1	1					y
0	0					!x
1	1					!y
0	0					-x
1	1					-y
0	1					x+1
1	1					y+1
0	0					x-1
1	1					y-1
0	0					x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	$x y$

Example: compute  $x|y$

x:        0 1 0 1

y:        0 0 1 1

Following pre-setting:

x:        1 0 1 0

y:        1 1 0 0

Computation and post-setting:

x&y:       1 0 0 0

!(x&y):    0 1 1 1

Practice:

See if you get

0 1 1 1 (bitwise Or)

# The Hack ALU operation: Compute $y-1$

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	
1	0	1	0	1	0	
1	1	1	1	1	1	
1	1	1	0	1	0	
0	0	1	1	0	0	
1	1	0	0	0	0	
0	0	1	1	0	1	
1	1	0	0	0	1	
0	0	1	1	1	1	
1	1	0	0	1	1	
0	1	1	1	1	1	
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

Practice:


See if you get

0 1 0 1 (5)

# The Hack ALU operation

---

One more detail:

 

if ( $\text{out} == 0$ ) then  $\text{zr} = 1$ , else  $\text{zr} = 0$

if ( $\text{out} < 0$ ) then  $\text{ng} = 1$ , else  $\text{ng} = 0$

The *zr* and *ng* output bits will come into play when we'll build the complete CPU architecture, later in the course.

# Chapter 2: Boolean Arithmetic

---

## Theory

- Representing numbers
- Binary numbers
- Boolean arithmetic
- Signed numbers

## Practice



Arithmetic Logic Unit (ALU)



Project 2: Chips

- Project 2: Guidelines

# Project 2

---

Given: All the chips built in Project 1


Goal: Build the chips:

- HalfAdder
- FullAdder
- Add16
- Inc16
- ALU



# Half Adder

---

 

a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


HalfAdder.hdl

```
/** Computes the sum of two bits. */  
CHIP HalfAdder {  
    IN a, b;  
    OUT sum, carry;  
    PARTS:  
        // Put your code here:  
}
```

## Implementation tip

Can be built from two  
gates built in project 1.

# Full Adder

 

a	b	c	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


FullAdder.hdl

```
/** Computes the sum of three bits. */  
CHIP FullAdder {  
    IN a, b, c;  
    OUT sum, carry;  
    PARTS:  
        // Put your code here:  
}
```

## Implementation tip

Can be built from two  
half-adders.

# 16-bit adder

 

Add16.hdl

```
/* Adds two 16-bit, two's-complement values.
   The most-significant carry bit is ignored. */
CHIP Add16 {
    IN a[16], b[16];
    OUT out[16];
    PARTS:
        // Put you code here:
}
```


- The bitwise additions are done in parallel
- The carry propagation is sequential
- Yet... it works fine, as is.  
How? Stay tuned for chapter 3.

## Implementation note

If you need to set a pin  $x$  to 0 (or 1) in HDL,  
use:  $x = \text{false}$  (or  $x = \text{true}$ )

# 16-bit incrementor

---

 


Inc16.hdl

```
/** Outputs in + 1. */  
CHIP Inc16 {  
    IN in[16];  
    OUT out[16];  
    PARTS:  
    // Put your code here:  
}
```


Implementation:  
Simple.

# ALU

 

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

# ALU

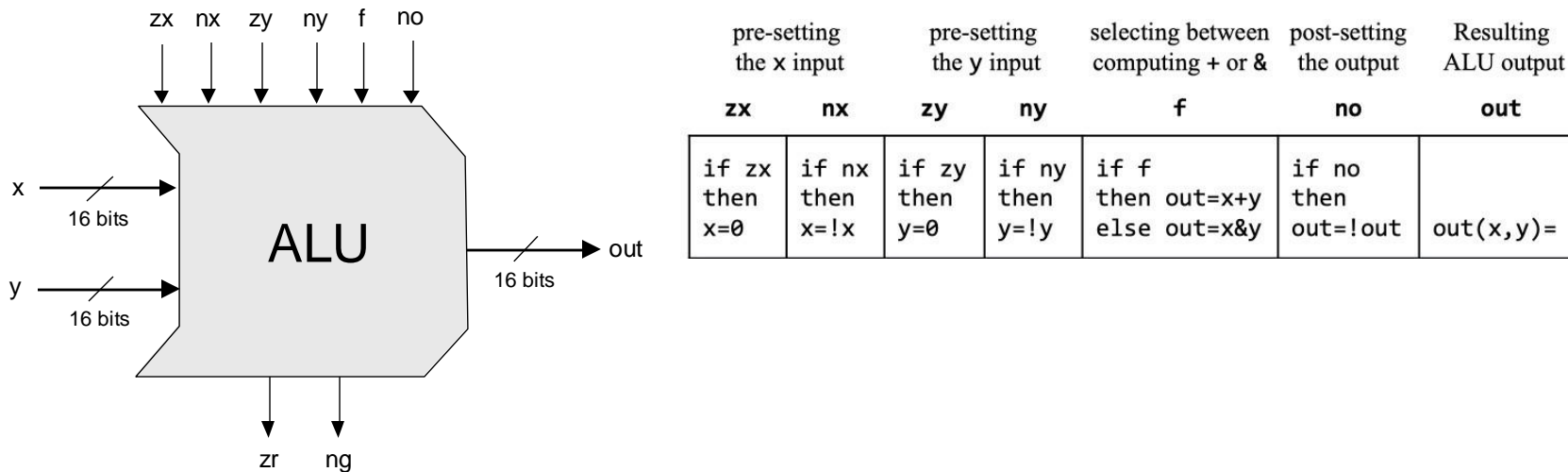


ALU.hdl

```

/** The ALU */
// Manipulates the x and y inputs as follows:
// if (zx == 1) sets x = 0           // 16-bit true
// if (nx == 1) sets x = !x         // 16-bit Not
// if (zy == 1) sets y = 0           // 16-bit true
// if (ny == 1) sets y = !y         // 16-bit Not
// if (f == 1) sets out = x + y     // 2's-complement addition
// if (f == 0) sets out = x & y     // 16-bit And
// if (no == 1) sets out = !out      // 16-bit Not
// if (out == 0) sets zr = 1         // 1-bit true
// if (out < 0) sets ng = 1          // 1-bit true
    
```

# ALU

 

ALU.hdl

```
/** The ALU */  
// Manipulates the x and y inputs as follows:  
// if (zx == 1) sets x = 0           // 16-bit true  
// if (nx == 1) sets x = !x         // 16-bit Not  
// if (zy == 1) sets y = 0           // 16-bit true  
// if (ny == 1) sets y = !y         // 16-bit Not  
// if (f == 1) sets out = x + y     // 2's-complement addition  
// if (f == 0) sets out = x & y     // 16-bit And  
// if (no == 1) sets out = !out      // 16-bit Not  
// if (out == 0) sets zr = 1         // 1-bit true  
// if (out < 0) sets ng = 1          // 1-bit true
```

## Implementation tips

We need logic for:

- Implementing “if bit == 0/1” conditions
- Setting a 16-bit value to 0000000000000000
- Setting a 16-bit value to 1111111111111111
- Negating a 16-bit value (bitwise)
- Computing Add and or on two 16-bit values

## Implementation strategy

- Start by building an ALU that computes out
- Next, extend it to also compute zr and ng.

# Relevant bus tips

Using multi-bit truth / false constants:

...

// Suppose that x, y, z are 8-bit bus-pins:

```
chipPart(..., x=true, y=false, z[0..2]=true, z[6..7]=true);
```

...

We can assign values to sub-buses

	7	6	5	4	3	2	1	0
x:	1	1	1	1	1	1	1	1
y:	0	0	0	0	0	0	0	0
z:	1	1	0	0	0	1	1	1

Unassigned bits are set to 0



# Relevant bus tips

---

Sub-bussing:

- We can assign  $n$ -bit values to sub-buses, for any  $n$
- We can create  $n$ -bit bus pins, for any  $n$

```
/* 16-bit adder */
```

```
CHIP Add16 {  
  IN a[16], b[16];  
  OUT out[16];  
}
```

```
PARTS:
```

```
...
```

```
}
```

```
CHIP Foo {
```

```
  IN x[8], y[8], z[16]
```

```
  OUT out[16]
```

```
  PARTS
```

```
  ...
```

```
  Add16 (a[0..7]=x, a[8..15]=y, b=z, out=...);
```

```
  ...
```

```
  Add16 (a=..., b=..., out[0..3]=t1, out[4..15]=t2);
```

```
  ...
```


```
}
```

Another example of assigning  
a multi-bit value to a sub-bus

Creating an  $n$ -bit bus (internal pin)

# ALU: Recap

---

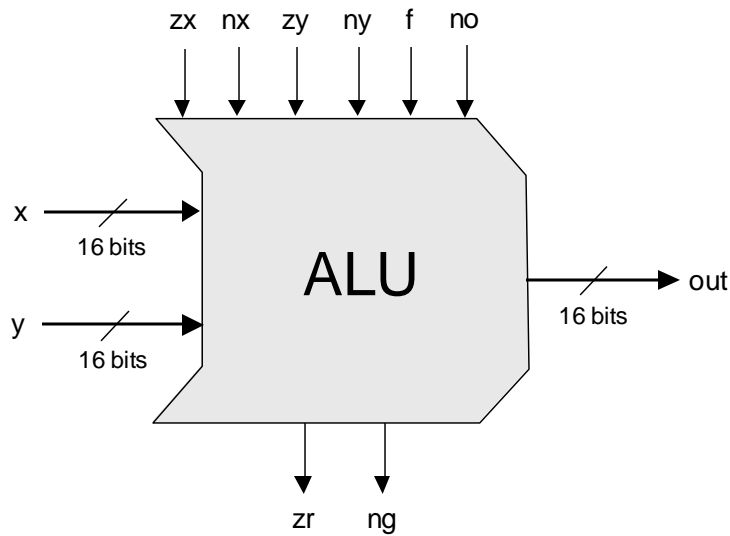

The Hack ALU is:

- Simple
- Elegant

“Simplicity is the  
ultimate sophistication.”  
— Leonardo da Vinci

# Chapter 2: Boolean Arithmetic

---

## Theory

- Representing numbers
- Binary numbers
- Boolean arithmetic
- Signed numbers


## Practice



Arithmetic Logic Unit (ALU)



Project 2: Chips

 

Project 2: Guidelines

# Project 2

---


Given: All the chips built in Project 1

Goal: Build the chips:

- HalfAdder
- FullAdder
- Add16
- Inc16
- ALU

# Guidelines: [www.nand2tetris.org/project02](http://www.nand2tetris.org/project02)

From NAND to Tetris  
Building a Modern Computer From First Principles  
[www.nand2tetris.org](http://www.nand2tetris.org)



Home  
Prerequisites  
Syllabus  
**Course**  
Book  
Software  
Terms  
Papers  
Talks  
Cool Stuff  
About  
Team  
Q&A

## Project 2: Combinational Chips

### Background

The centerpiece of the computer's architecture is the *CPU*, or *Central Processing Unit*, and the centerpiece of the CPU is the *ALU*, or *Arithmetic-Logic Unit*. In this project you will gradually build a set of chips, culminating in the construction of the *ALU* chip of the *Hack* computer. All the chips built in this project are standard, except for the *ALU* itself, which differs from one computer architecture to another.

### Objective

Build all the chips described in Chapter 2 (see list below), leading up to an *Arithmetic Logic Unit* - the Hack computer's *ALU*. The only building blocks that you can use are the chips described in chapter 1 and the chips that you will gradually build in this project.

### Chips

Chip (HDL)	Description	Test script	Compare file
HalfAdder	Half Adder	HalfAdder.tst	HalfAdder.cmp
FullAdder	Full Adder	FullAdder.tst	FullAdder.cmp
Add16	16-bit Adder	Add16.tst	Add16.cmp
Inc16	16-bit incrementer	Inc16.tst	Inc16.cmp
ALU	Arithmetic Logic Unit	ALU.tst	ALU.cmp

# Resources

---

Project 2 folder (.hdl, .tst, .cmp files):  
nand2tetris/projects/02

## Tools

- Text editor (for completing the given .hdl stub-files)
- Hardware simulator: nand2tetris/tools

## Guides

- [Hardware Simulator Tutorial](#)
- [HDL Guide](#)
- [Hack Chip Set API](#)

# Chip interfaces: [Hack chip set API](#)

Open the API in a window, and copy-paste chip signatures into your HDL code, as needed

```
Add16 (a= ,b= ,out= );
ALU (x= ,y= ,zx= ,nx= ,zy= ,ny= ,f= ,no= ,out= ,zr= ,ng= );
And16 (a= ,b= ,out= );
And (a= ,b= ,out= );
Aregister (in= ,load= ,out= );
Bit (in= ,load= ,out= );
CPU (inM= ,instruction= ,reset= ,outM= ,writeM= ,address= );
DFF (in= ,out= );
DMux4Way (in= ,sel= ,a= ,b= ,c= ,d= );
DMux8Way (in= ,sel= ,a= ,b= ,c= ,d= ,e= ,f= ,g= ,h= );
Dmux (in= ,sel= ,a= ,b= );
Dregister (in= ,load= ,out= );
FullAdder (a= ,b= ,c= ,sum= ,carry= );
HalfAdder (a= ,b= ,sum= , carry= );
Inc16 (in= ,out= );
Keyboard (out= );
Memory (in= ,load= ,address= ,out= );
Mux16 (a= ,b= ,sel= ,out= );
Mux4Way16 (a= ,b= ,c= ,d= ,sel= ,out= );
Mux8Way16 (a= ,b= ,c= ,d= ,e= ,f= ,g= ,h= ,sel= ,out= );
```

```
Mux8Way (a= ,b= ,c= ,d= ,e= ,f= ,g= ,h= ,sel= ,out= );
Mux (a= ,b= ,sel= ,out= );
Nand (a= ,b= ,out= );
Not16 (in= ,out= );
Not (in= ,out= );
Or16 (a= ,b= ,out= );
Or8Way (in= ,out= );
Or (a= ,b= ,out= );
PC (in= ,load= ,inc= ,reset= ,out= );
PCLoadLogic (cinstr= ,j1= ,j2= ,j3= ,load= ,inc= );
RAM16K (in= ,load= ,address= ,out= );
RAM4K (in= ,load= ,address= ,out= );
RAM512 (in= ,load= ,address= ,out= );
RAM64 (in= ,load= ,address= ,out= );
RAM8 (in= ,load= ,address= ,out= );
Register (in= ,load= ,out= );
ROM32K (address= ,out= );
Screen (in= ,load= ,address= ,out= );
Xor (a= ,b= ,out= );
```

# Best practice advice

---


- Implement the chips in the order in which they appear in the project guidelines
- If you don't implement some chips, you can still use their built-in implementations
- No need for “helper chips”: Implement / use only the chips we specified
- In each chip definition, strive to use as few chip-parts as possible
- You will have to use chips implemented in Project 1;  
For efficiency and consistency's sake, use their built-in versions, rather than your own HDL implementations.

That's It!

Go Do Project 2!



# What's next?

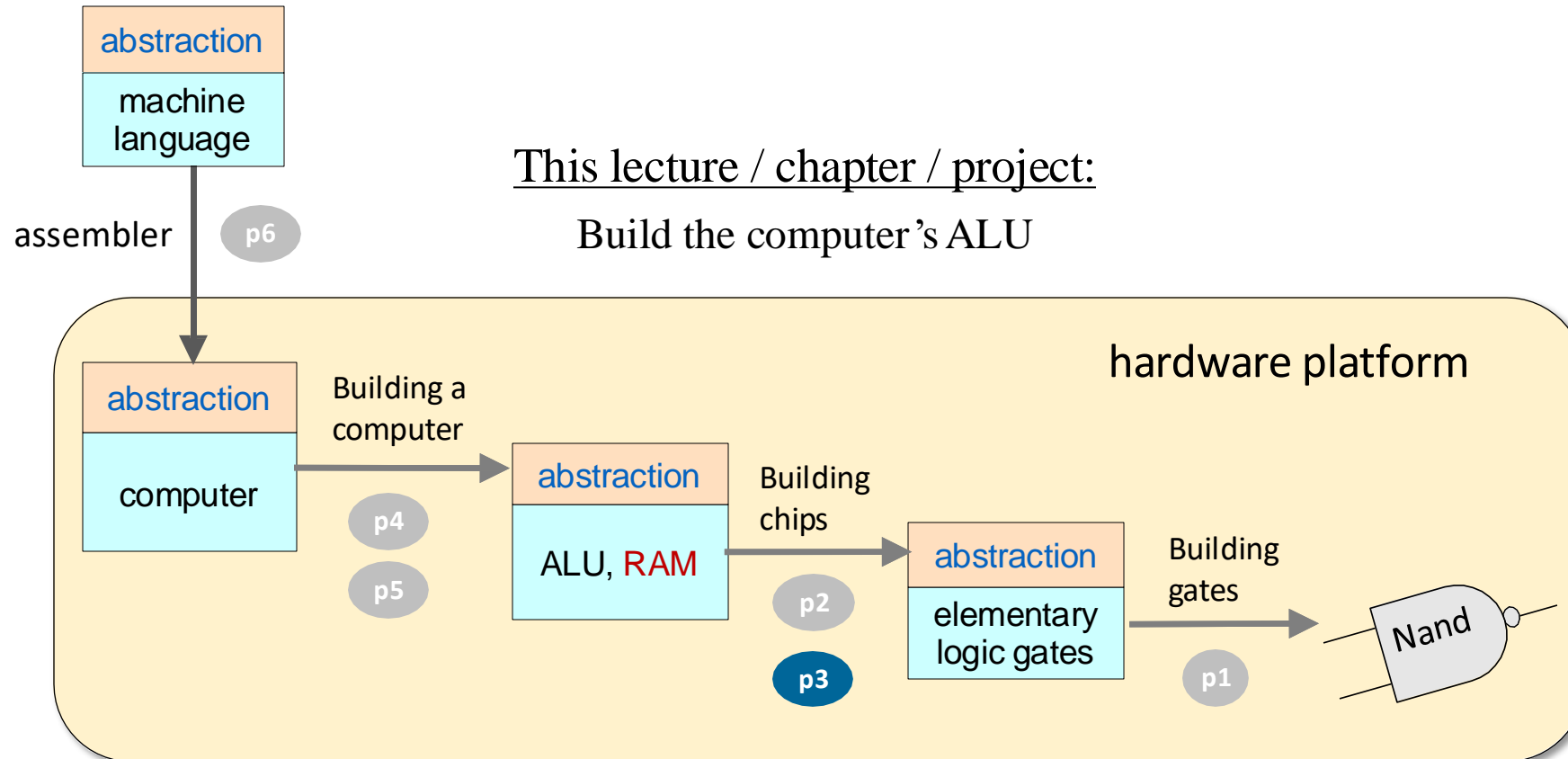

Next lecture / chapter / project:

Build the computer's RAM