

# *22AIE114 : Introduction to Electrical and Electronic Engineering (2-0-3-3)*



## *Unit 1, Lecture 4*



*Topic: Star Delta Transformation and Series – parallel capacitors, inductors*

# Outline

- To understand star-delta transformations.
- To understand series and parallel combinations of capacitors
- To understand series and parallel combinations of Inductors
- To perform network reductions and solving circuits.

# Star (Y) - Delta Transformation
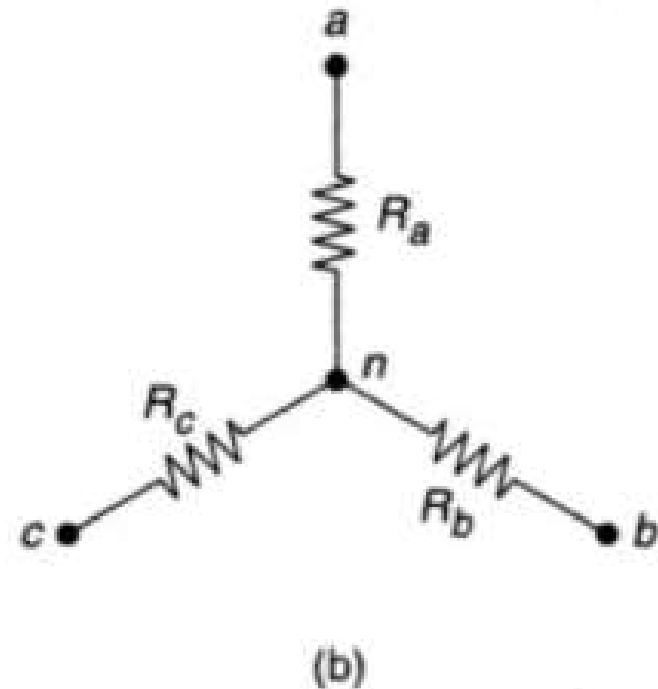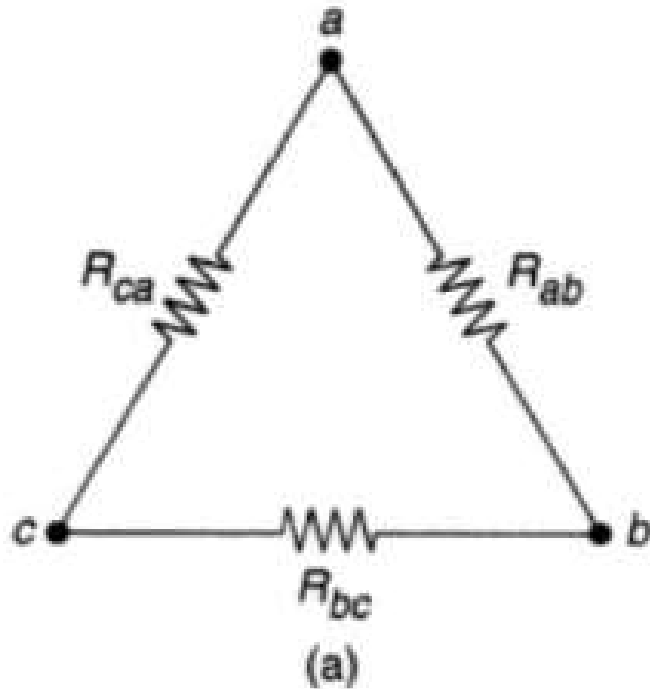
## STAR (Y)-DELTA ( $\Delta$ ) CONVERSION



(a) Delta-connected and (b) Star-connected networks


# Star - Delta Transformation

Certain network configurations cannot be resolved by series-parallel combinations alone. Such configurations are handled by  $Y$ - $\Delta$  transformations.

Figure (a) shows three  $\Delta$ -connected resistances connected between three nodes  $a$ ,  $b$  and  $c$ .

Fig. (b), there are three  $Y$ -connected resistances.  
 $Y$ -connection has an extra node  $n$  that gets eliminated upon converting it to  $\Delta$ .  
 $Y$ - $\Delta$  conversion is therefore a *node reduction* technique.

# Star - Delta Transformation

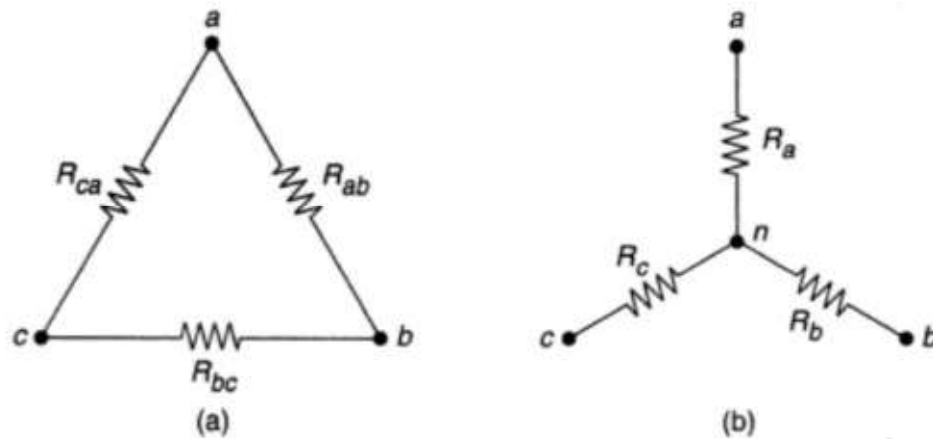

(a) Delta-connected and (b) Star-connected networks

Equating resistance between node pairs:

Node pair  $ab$

$$R_a + R_b = R_{ab} \parallel (R_{bc} + R_{ca})$$

Node pair  $bc$

$$R_b + R_c = R_{bc} \parallel (R_{ca} + R_{ab})$$

Node pair  $ca$

$$R_c + R_a = R_{ca} \parallel (R_{ab} + R_{bc})$$

# Star - Delta Transformation

Solving above 3 equations, we get:

*Y-Δ Conversion*

$$R_{ab} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_{bc} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$$R_{ca} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

*Δ-Y Conversion*

$$R_a = \frac{R_{ab} R_{ac}}{R_{ab} + R_{bc} + R_{ca}}$$

$$R_b = \frac{R_{bc} R_{ba}}{R_{ab} + R_{bc} + R_{ca}}$$


$$R_c = \frac{R_{ca} R_{cb}}{R_{ab} + R_{bc} + R_{ca}}$$

*Balanced Y-Δ*


A balanced Y ( $R_a = R_b = R_c = R_Y$ ) leads to balanced Δ ( $R_{ab} = R_{bc} = R_{ca} = R_{\Delta}$ ) wherein

$$R_{\Delta} = 3R_Y$$

# Star - Delta Transformation

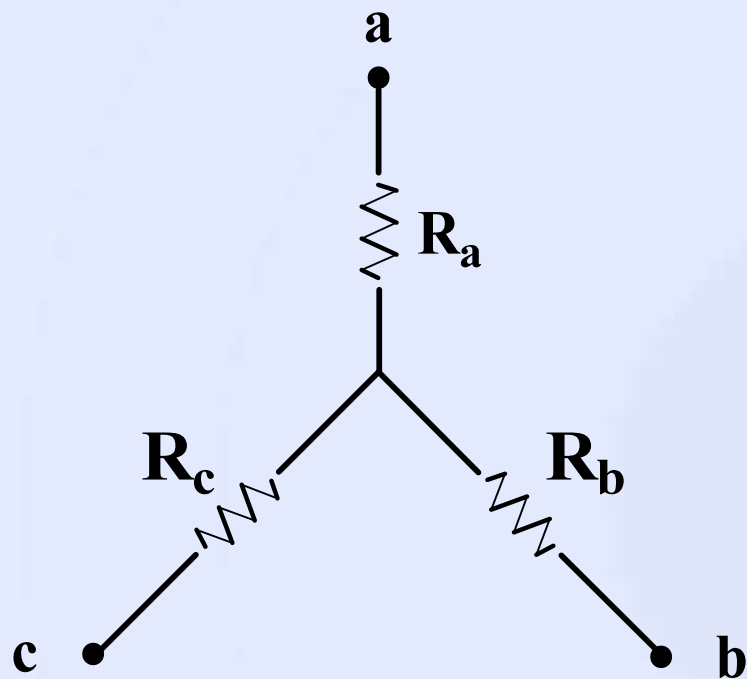

**(a) wye configuration**

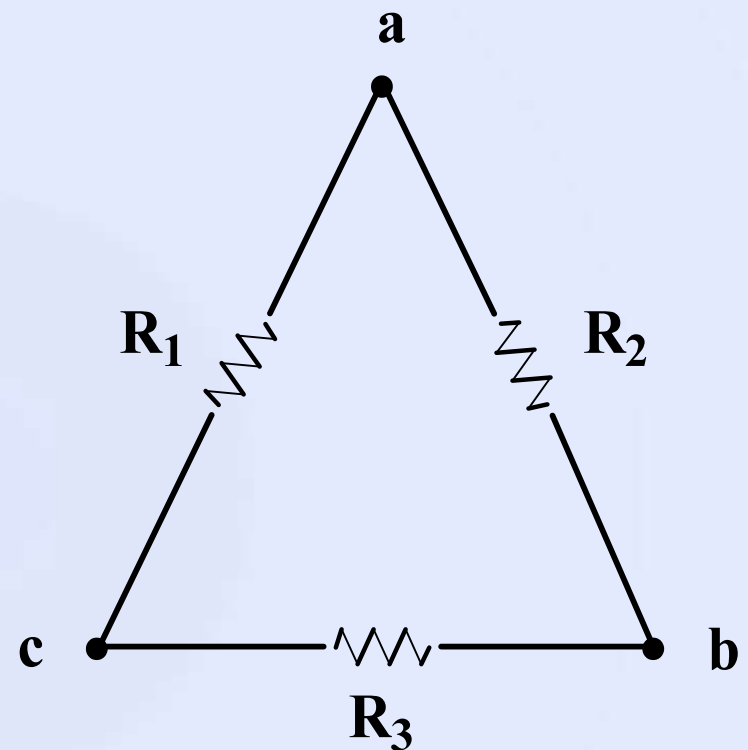

**(b) delta configuration**

# Star - Delta Transformation

**Go to wye**

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

**Go to delta**

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$


$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

**We note that the denominator for  $R_a$ ,  $R_b$ ,  $R_c$  is the same.  
We note that the numerator for  $R_1$ ,  $R_2$ ,  $R_3$  is the same.**


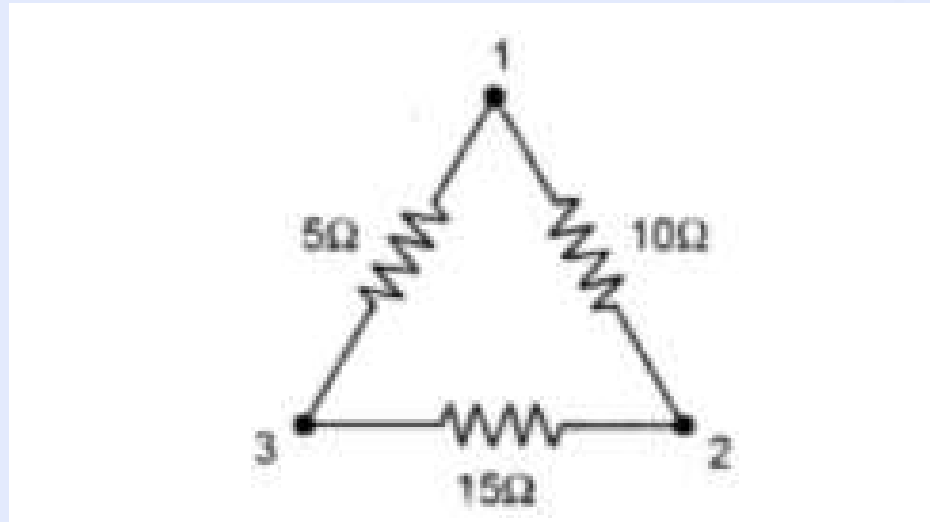
# Example 1

Convert given delta circuit to equivalent star




**Solution :**

$$R_1 = \frac{10 \times 5}{5 + 10 + 15} = 1.67 \, \Omega$$


$$R_2 = \frac{15 \times 10}{5 + 10 + 15} = 5 \, \Omega$$
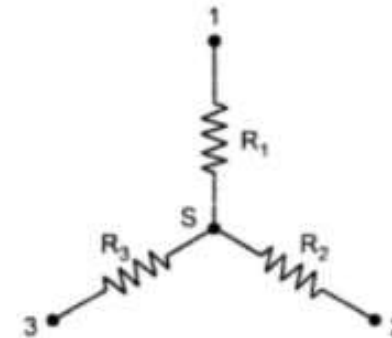
$$R_3 = \frac{5 \times 15}{5 + 10 + 15} = 2.5 \, \Omega$$



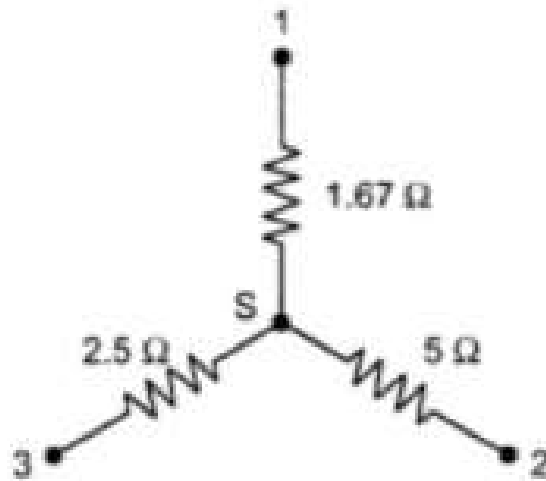
# Example 2

Convert given Star circuit to equivalent Delta



Solution :

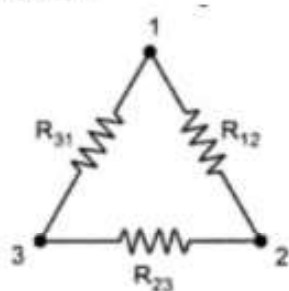


$$R_{12} = 1.67 + 5 + \frac{1.67 \times 5}{2.5} = 1.67 + 5 + 3.33 = 10 \Omega$$

$$R_{23} = 5 + 2.5 + \frac{5 \times 2.5}{1.67} = 5 + 2.5 + 7.5 = 15 \Omega$$

$$R_{31} = 2.5 + 1.67 + \frac{2.5 \times 1.67}{5} = 2.5 + 1.67 + 0.833 = 5 \Omega$$
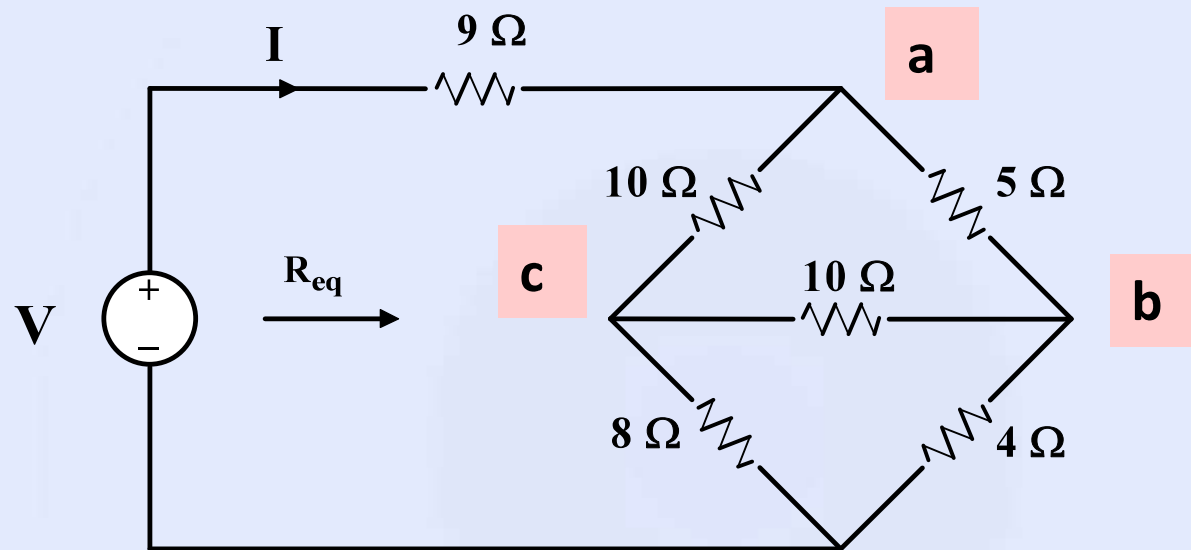
# Example 3


Find  $R_{eq}$  of the circuit in the given Figure




Convert the delta around  $a - b - c$  to a wye.
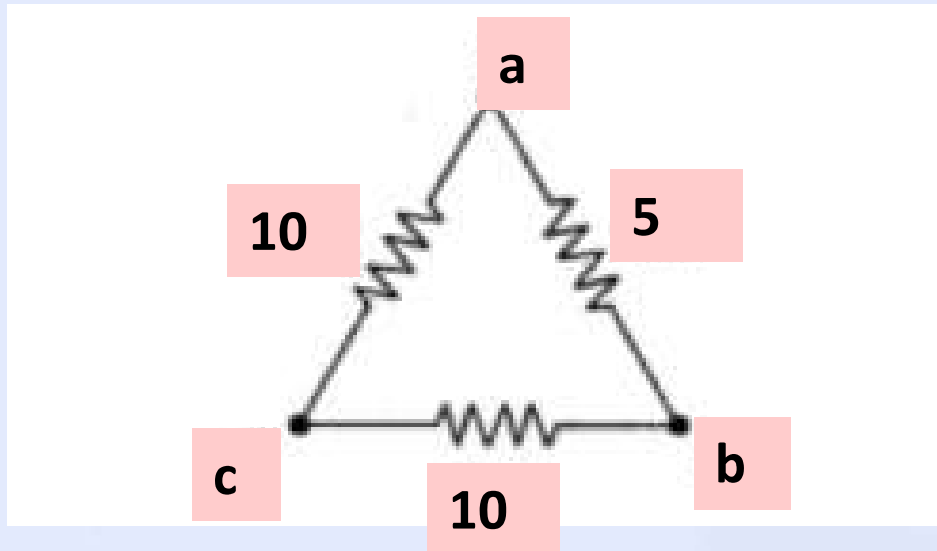
# Example 3

Find  $R_{eq}$  of the circuit in the given Figure



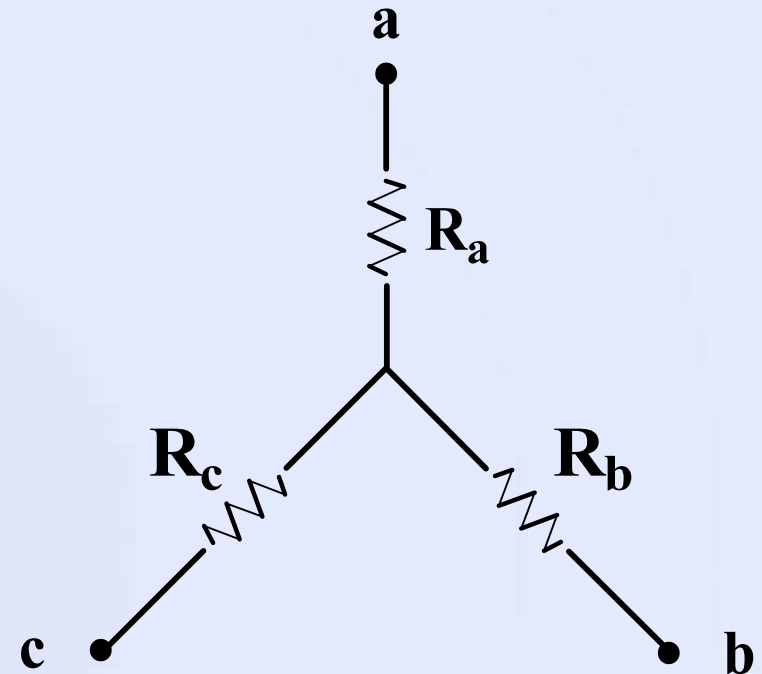
Convert the delta around a – b – c to a wye.



$$\begin{aligned} R_a &= 2 \text{ Ohms} \\ R_b &= 2 \text{ Ohms} \\ R_c &= 4 \text{ Ohms} \end{aligned}$$
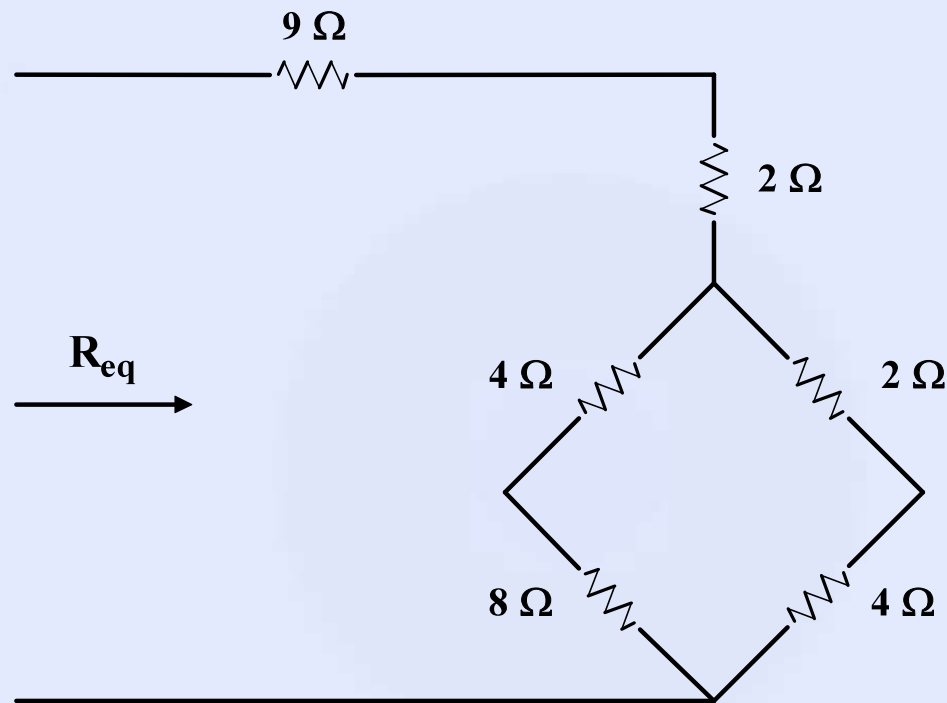
# Example 3


Find  $R_{eq}$  of the circuit in the given Figure



It is easy to see that  $R_{eq} = 15\ \Omega$

# Example 4



Using wye to delta, find  $R_{eq}$

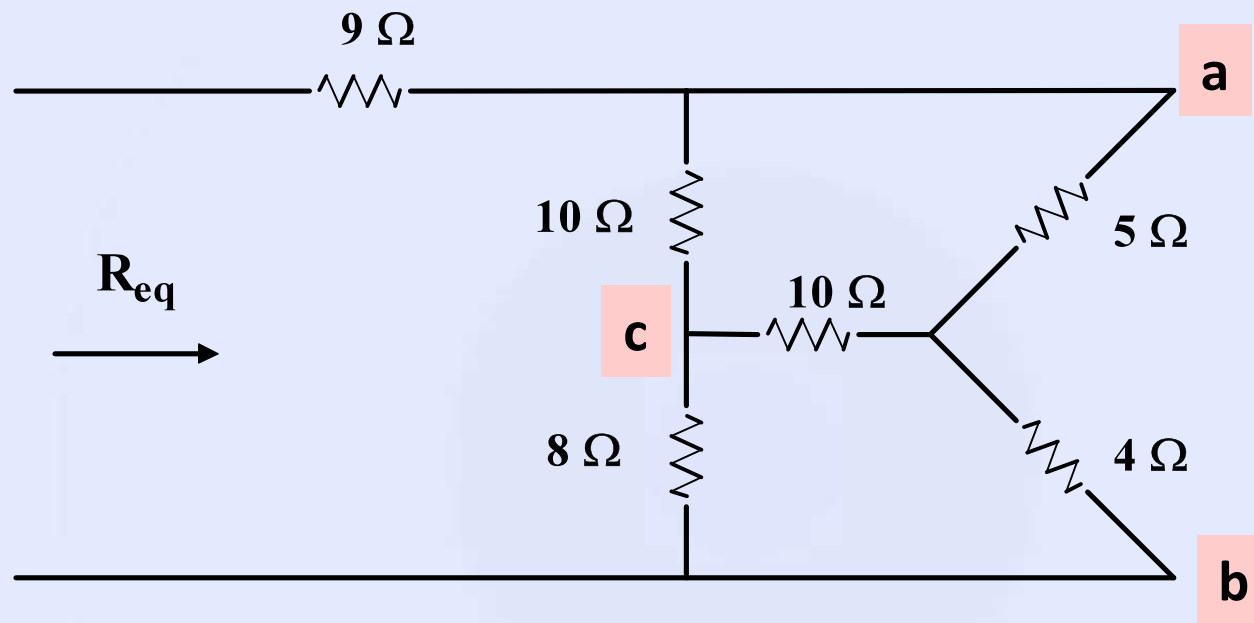

Convert star to delta at a-b-c


# Example 4

Using wye to delta, find  $R_{eq}$

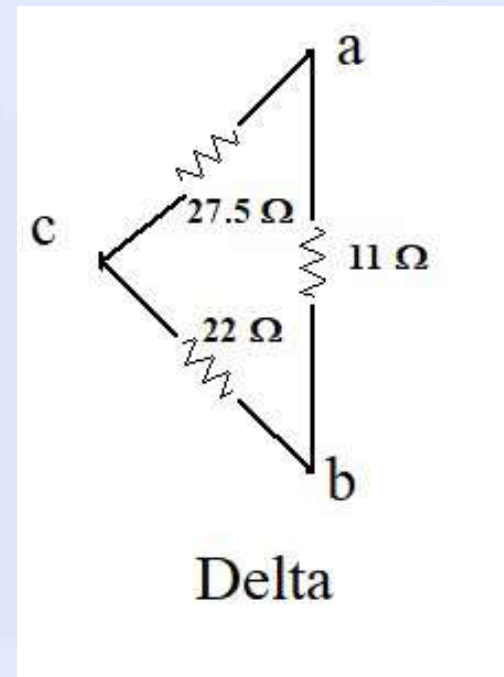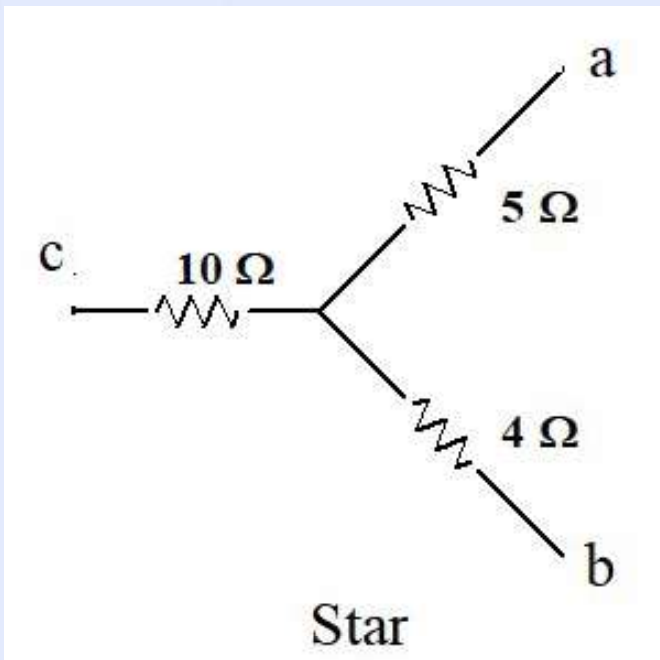


# Example 4

Using wye to delta, find  $R_{eq}$

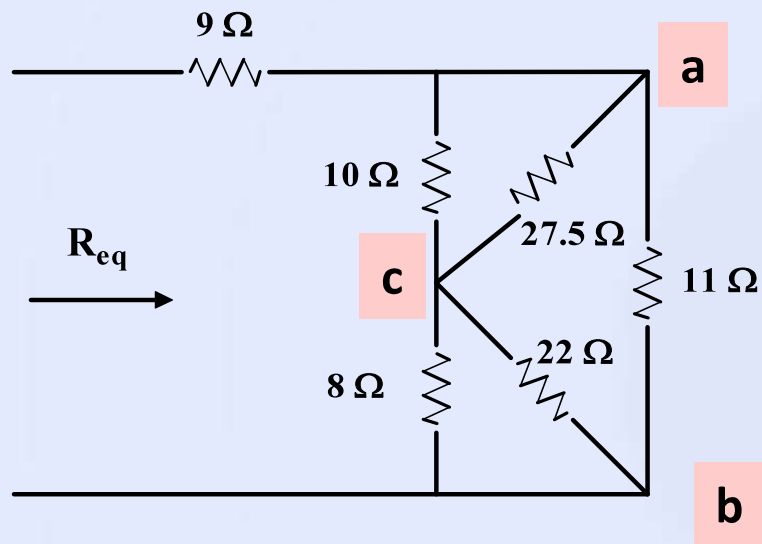

(a)

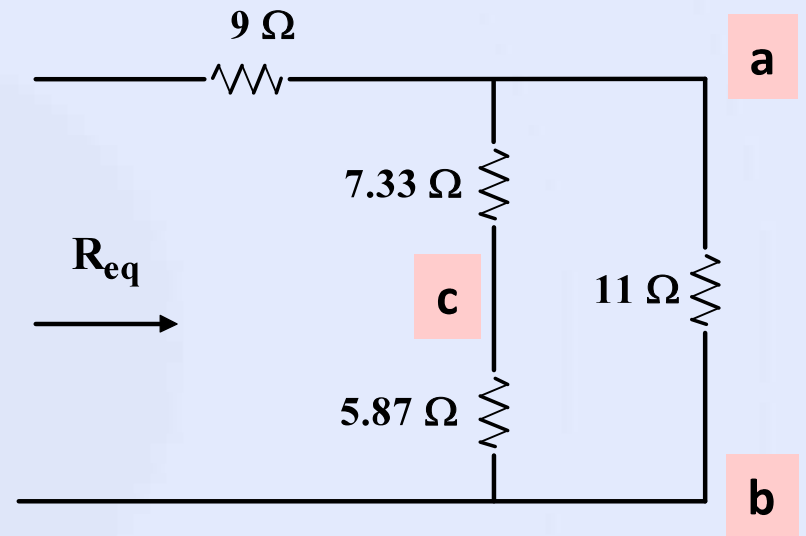


(b)



# Example 4


Using wye to delta, find  $R_{eq}$

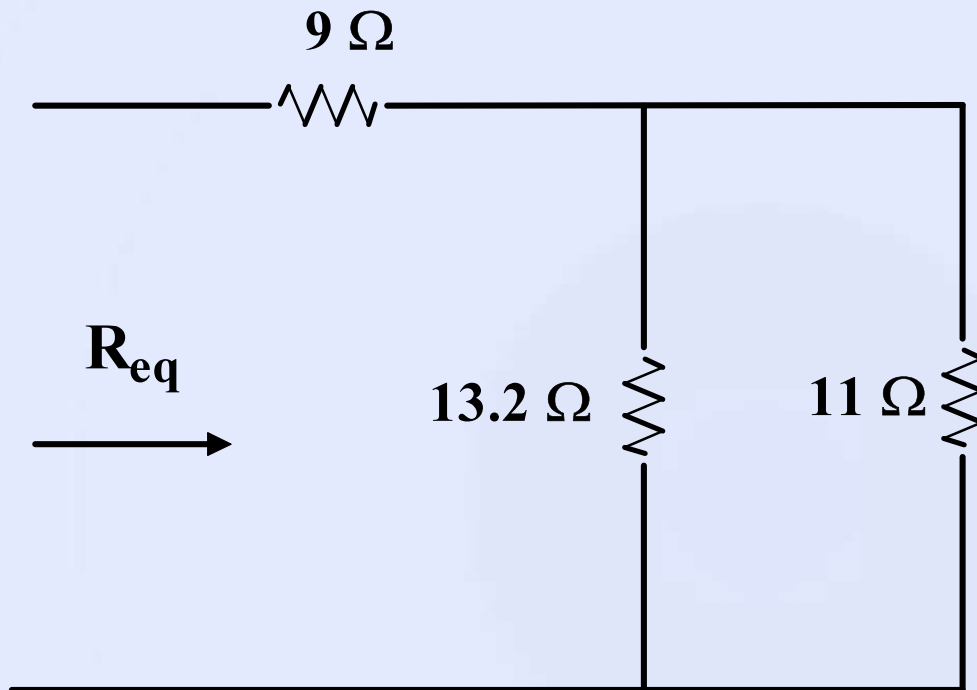

$$R_{eq} = 15\ \Omega$$
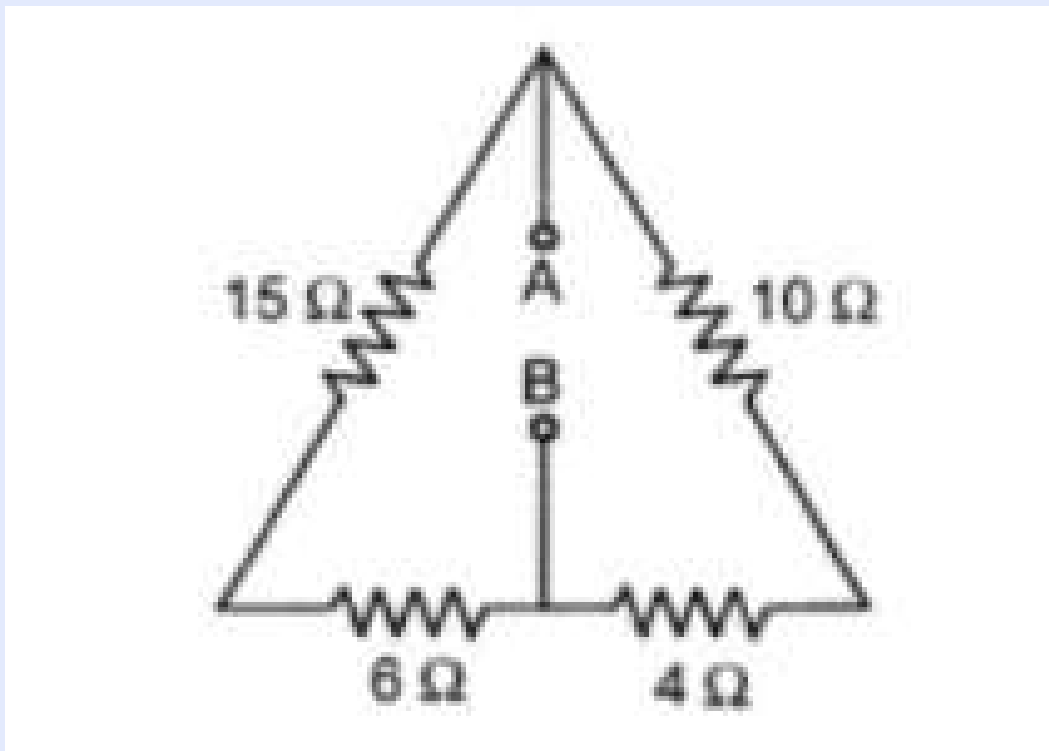
# Example 5


Find equivalent resistance between points A-B



# Example 5


Find equivalent resistance between points A-B

Redrawing the circuit

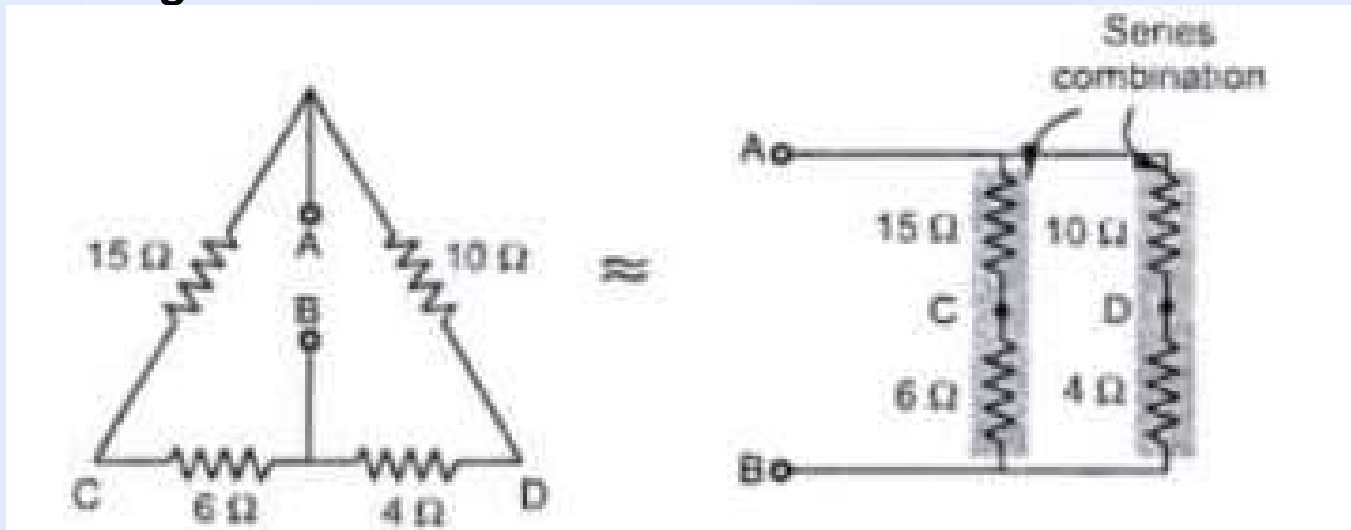

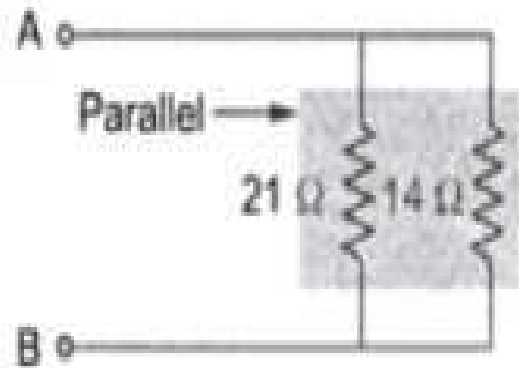
# Example 5

Find equivalent resistance between points A-B




$\approx$

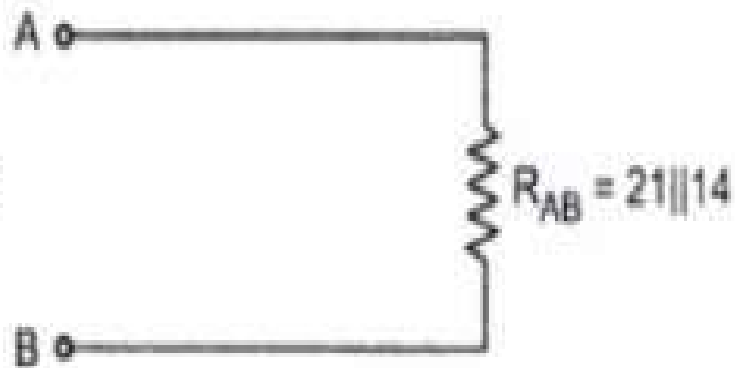

$$R_{AB} = \frac{21 \times 14}{21 + 14} = 8.4\ \Omega$$

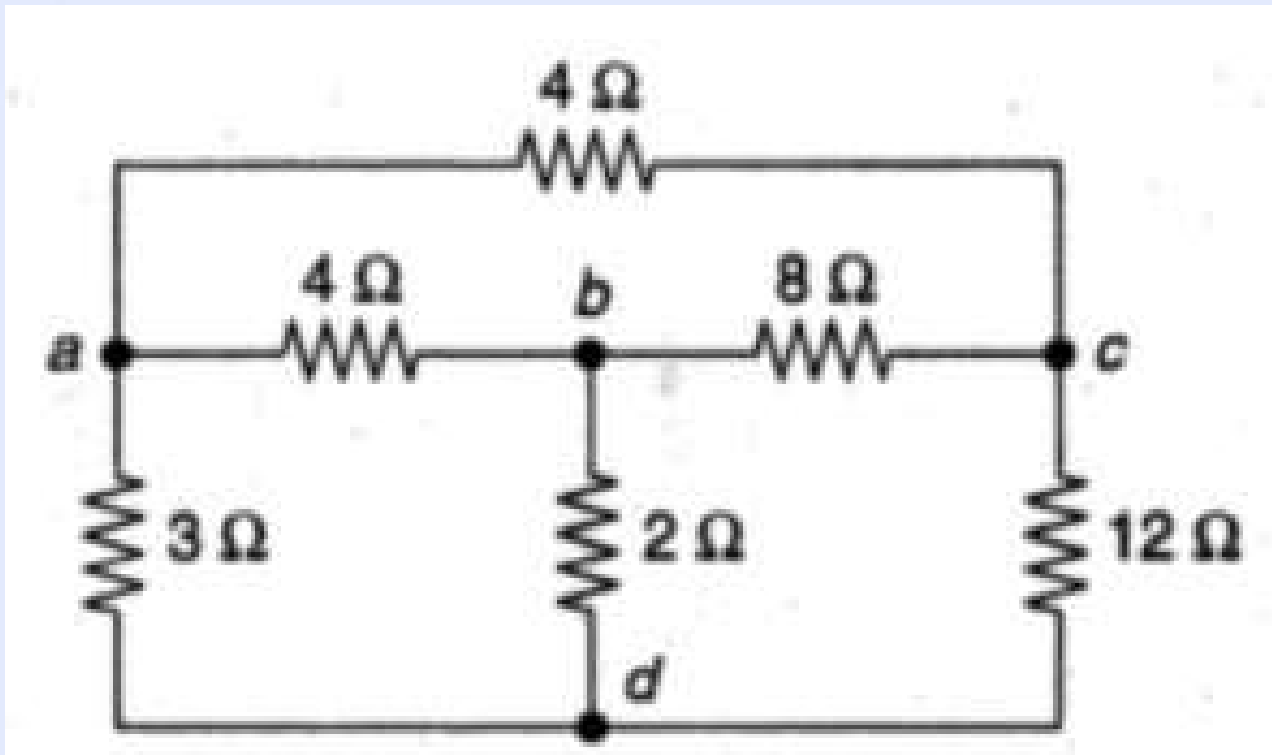
# Example 6

Calculate the equivalent resistance between nodes  $a$  and  $d$


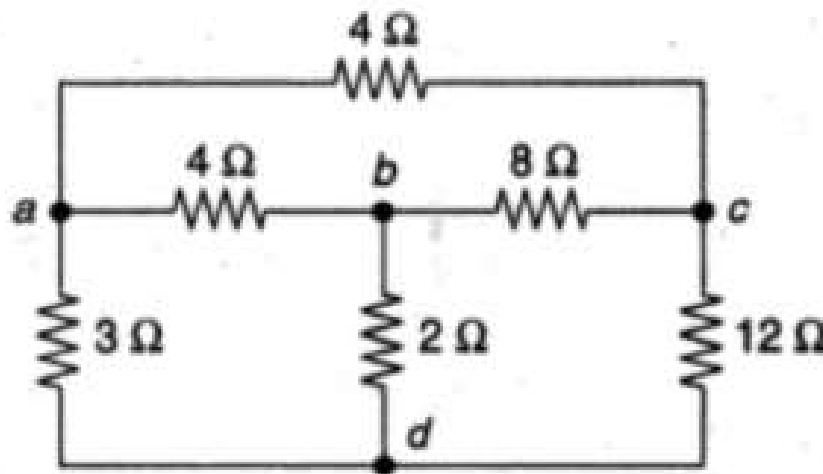
# Example 6

Calculate the equivalent resistance between nodes ad



## **Solution**

Converting the  $Y$  at node  $b$  to  $\Delta$ ,

$$R_x = \frac{4 \times 8 + 8 \times 2 + 2 \times 4}{2} = 28 \Omega$$

$$R_y = \frac{4 \times 8 + 8 \times 2 + 2 \times 4}{8} = 7 \Omega$$


$$R_z = \frac{4 \times 8 + 8 \times 2 + 2 \times 4}{4} = 14 \Omega$$

# Example 6

Calculate the equivalent resistance between nodes ad


By series-parallel combination, we get
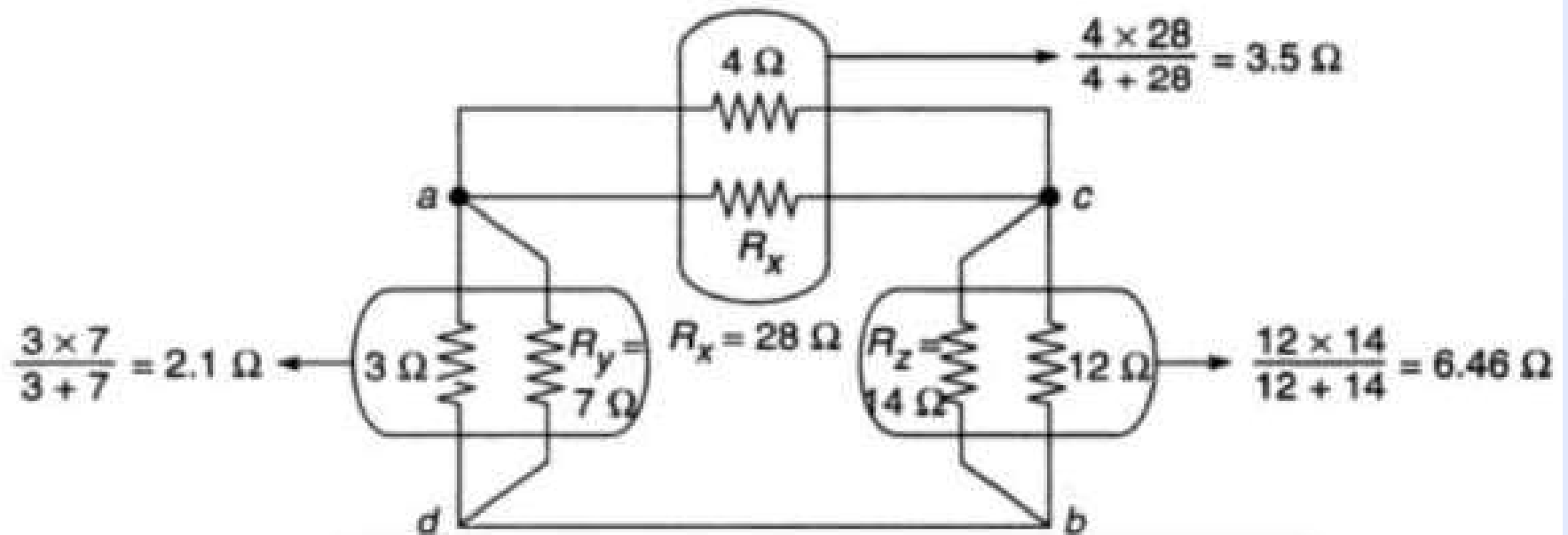
$$R_{ad}(\text{eq}) = \frac{2.1 \times (3.5 + 6.46)}{2.1 + 3.5 + 6.46} = 1.734 \Omega$$


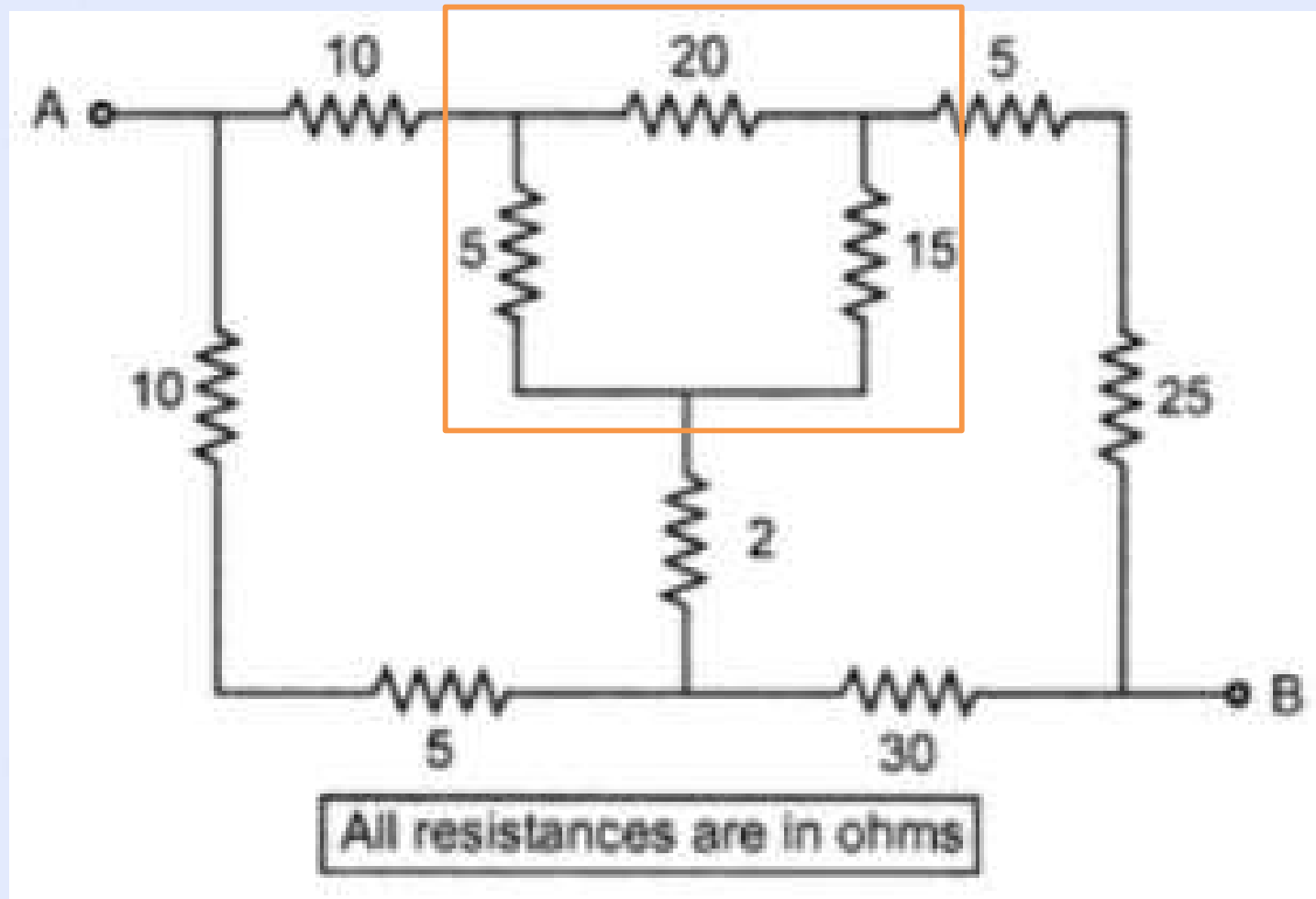
# Example 7


Find resistance between the terminals A-B of the circuit




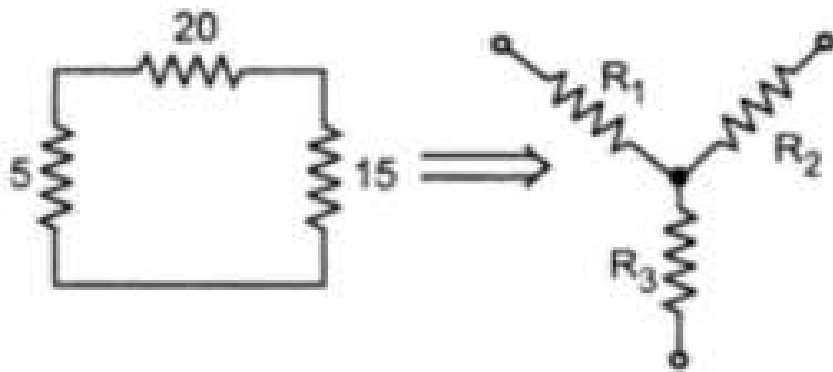
# Example 7

Find resistance between the terminals A-B of the circuit



(a)


$$R_1 = \frac{20 \times 5}{20 + 5 + 15} = 2.5 \, \Omega$$

$$R_2 = \frac{20 \times 15}{20 + 5 + 15} = 7.5 \, \Omega$$

$$R_3 = \frac{5 \times 15}{20 + 5 + 15} = 1.875 \, \Omega$$

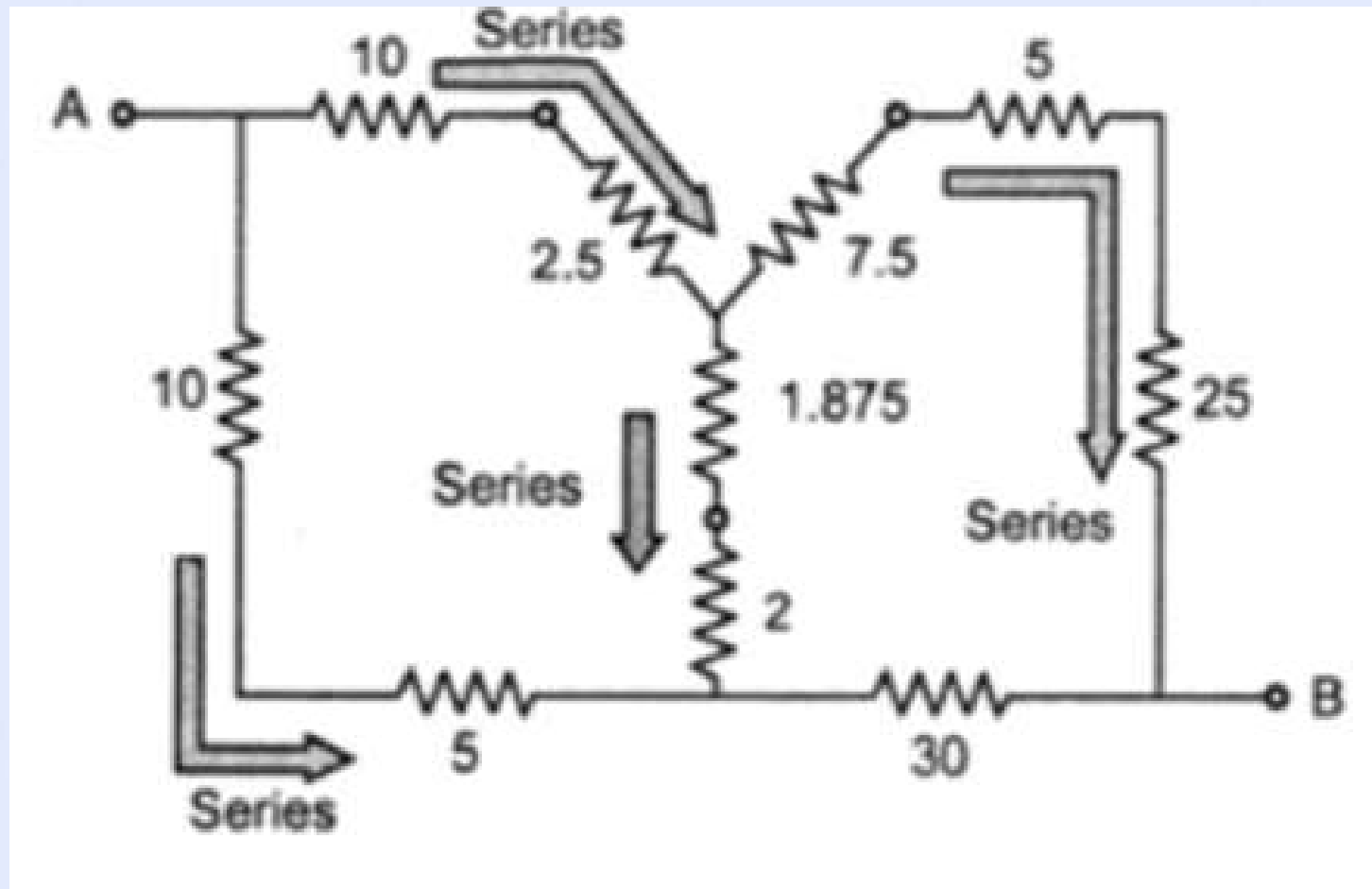
# Example 7

Find resistance between the terminals A-B of the circuit


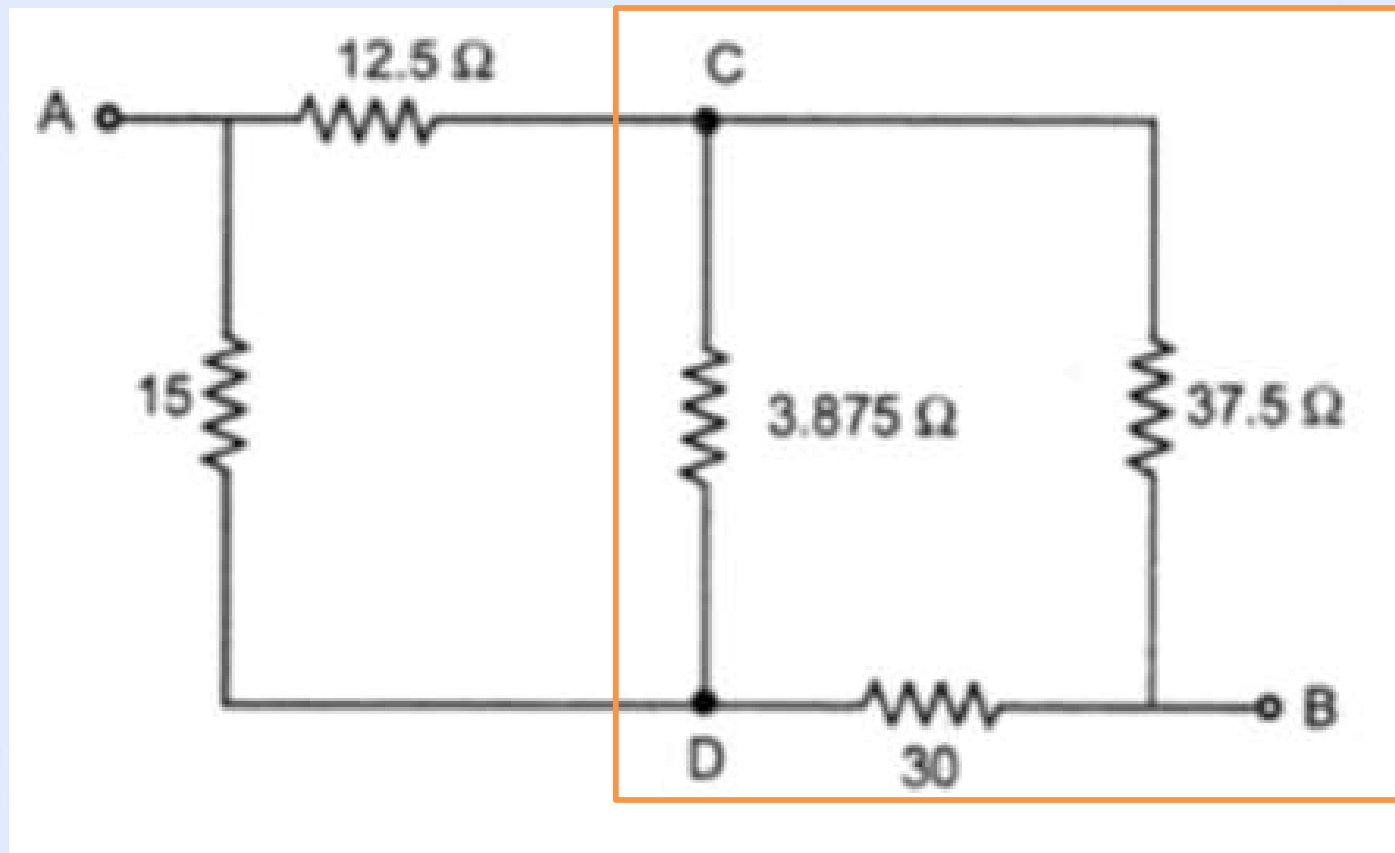
# Example 7


Find resistance between the terminals A-B of the circuit


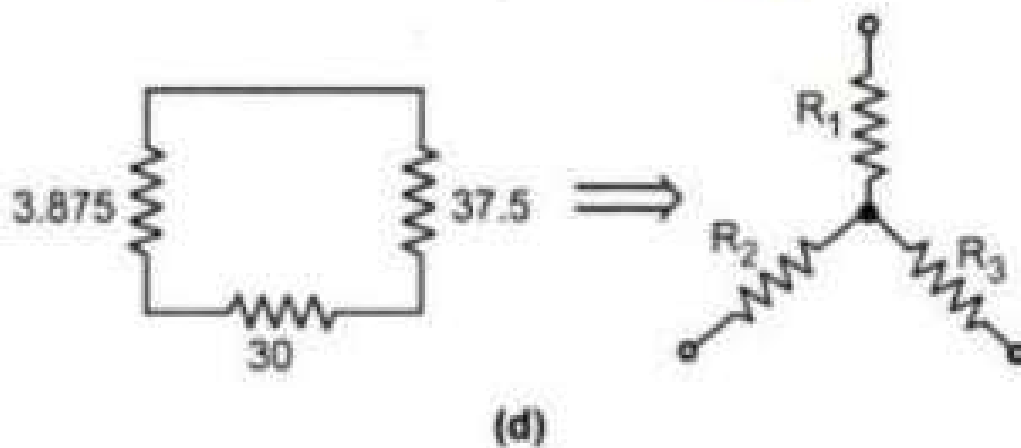
# Example 7

Find resistance between the terminals A-B of the circuit

Convert  $\Delta$  CDB to equivalent star,





$$R_1 = \frac{3.875 \times 37.5}{3.875 + 37.5 + 30} = 2.036 \Omega$$


$$R_2 = \frac{3.875 \times 30}{3.875 + 37.5 + 30} = 1.6287 \Omega$$

$$R_3 = \frac{30 \times 37.5}{3.875 + 37.5 + 30} = 15.7618 \Omega$$

# Example 7

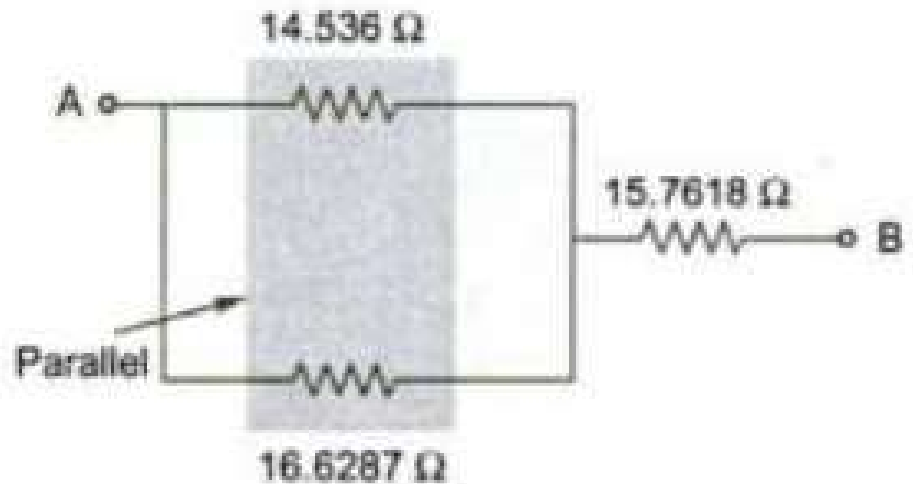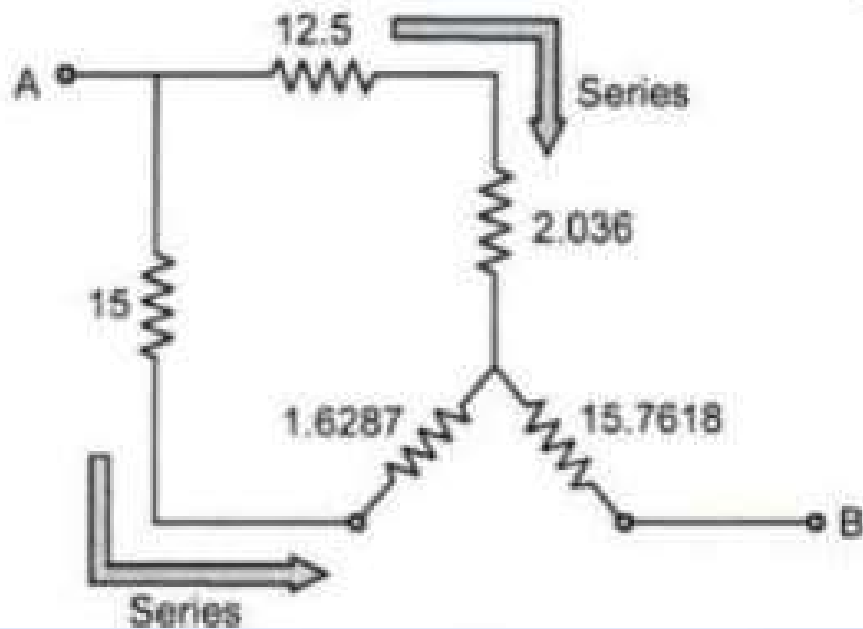**Find resistance between the terminals A-B of the circuit**






$$\frac{14.536 \times 16.6287}{14.536 + 16.6287} = 7.7557 \, \Omega$$

$$R_{AB} = 7.7557 + 15.7618$$
$$= 23.5175 \, \Omega$$
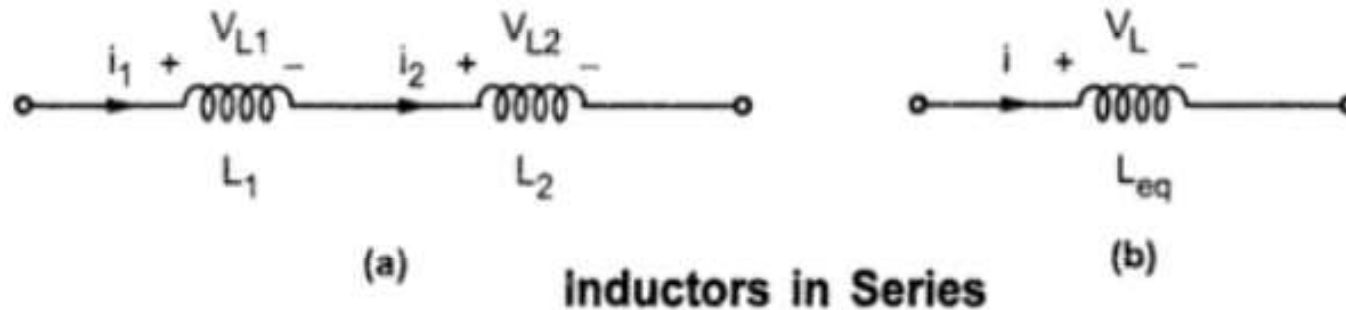
# Inductors in series

The currents flowing through  $L_1$  and  $L_2$  are  $i_1$  and  $i_2$  while voltages developed across  $L_1$  and  $L_2$  are  $V_{L1}$  and  $V_{L2}$  respectively.



We have,  $V_{L1} = L_1 \frac{di_1}{dt}$  and  $V_{L2} = L_2 \frac{di_2}{dt}$  while  $V_L = L_{eq} \frac{di}{dt}$

# Inductors in series

For series combination,

$$i = i_1 = i_2$$

and

$$V_L = V_{L1} + V_{L2}$$

$$\therefore L_{eq} \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$

$$\therefore L_{eq} \frac{di}{dt} = (L_1 + L_2) \frac{di}{dt}$$

$\therefore$

$$L_{eq} = L_1 + L_2$$


That means, equivalent inductance of the series combination of two inductances is the sum of inductances connected in series.

For n inductances in series,

$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_n$$
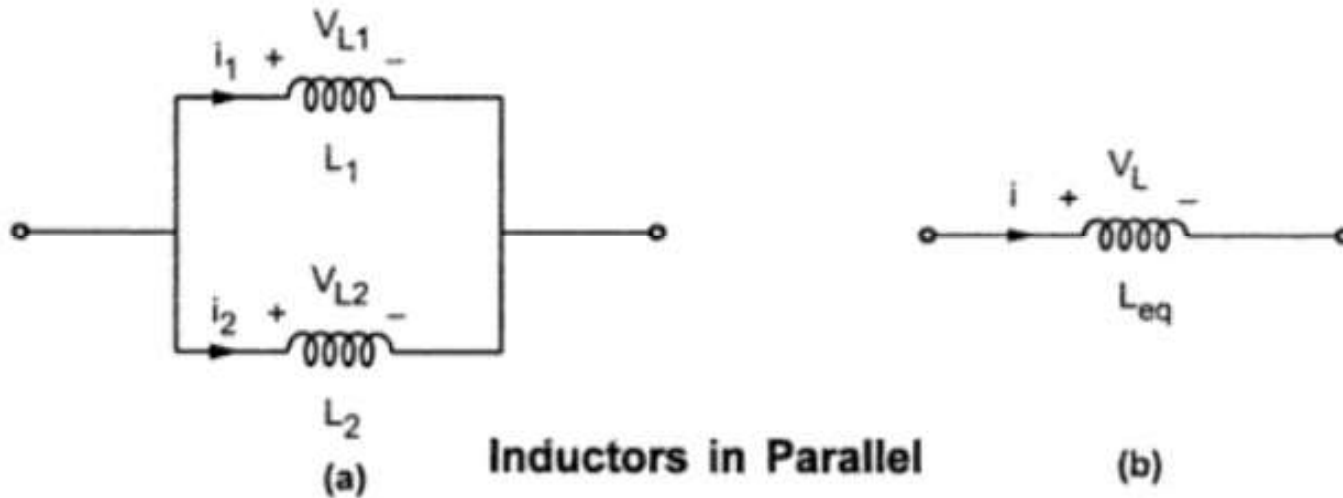
# Inductors in parallel

The currents flowing through  $L_1$  and  $L_2$  are  $i_1$  and  $i_2$  respectively. The voltage developed across  $L_1$  and  $L_2$  are  $V_{L1}$  and  $V_{L2}$  respectively.



For inductor we have,

$$i_1 = \frac{1}{L_1} \int_{-\infty}^t V_{L1} dt, \quad i_2 = \frac{1}{L_2} \int_{-\infty}^t V_{L2} dt, \quad \text{while} \quad i = \frac{1}{L_{eq}} \int_{-\infty}^t V_L dt$$



# Inductors in parallel

For parallel combination,

$$V_L = V_{L1} = V_{L2} \quad \text{and}$$

$$i = i_1 + i_2$$

$$\therefore \frac{1}{L_{eq}} \int_{-\infty}^t V_L dt = \frac{1}{L_1} \int_{-\infty}^t V_L dt + \frac{1}{L_2} \int_{-\infty}^t V_L dt = \left( \frac{1}{L_1} + \frac{1}{L_2} \right) \int_{-\infty}^t V_L dt$$

$$\therefore \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

That means, reciprocal of equivalent inductance of the parallel combination is the sum of reciprocals of the individual inductances.


For  $n$  inductances in parallel,

$\therefore$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

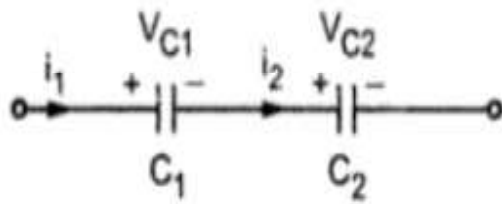
# Capacitors in series

The currents flowing through and voltages developed across  $C_1$  and  $C_2$  are  $i_1$ ,  $i_2$  and  $V_{C1}$  and  $V_{C2}$  respectively.



(a)

Capacitors in series

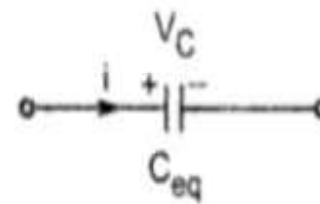

(b)

$$\text{We have, } V_{C1} = \frac{1}{C_1} \int_{-\infty}^t i_1 dt, \quad V_{C2} = \frac{1}{C_2} \int_{-\infty}^t i_2 dt \quad \text{while} \quad V = \frac{1}{C_{eq}} \int_{-\infty}^t i dt$$

# Capacitors in series

For series combination,

$$i = i_1 = i_2 \quad \text{and}$$

$$V_C = V_{C1} + V_{C2}$$

$$\frac{1}{C_{eq}} \int_{-\infty}^t i dt = \frac{1}{C_1} \int_{-\infty}^t i_1 dt + \frac{1}{C_2} \int_{-\infty}^t i_2 dt$$

But

$$i = i_1 = i_2$$

$$\therefore \frac{1}{C_{eq}} \int_{-\infty}^t i dt = \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \int_{-\infty}^t i dt$$

$$\therefore \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\therefore \boxed{C_{eq} = \frac{C_1 C_2}{C_1 + C_2}}$$


For n capacitors in series,

$$\boxed{\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n}}$$

That means, reciprocal of equivalent capacitor of the series combination is the sum of the reciprocal of individual capacitances.

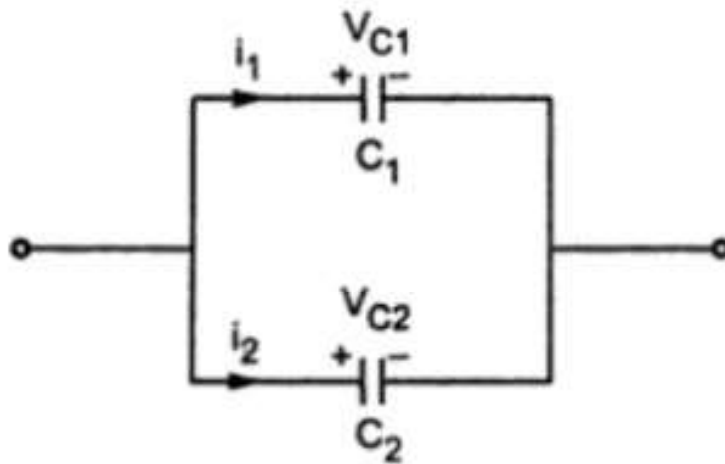
# Capacitors in parallel

The currents flowing through  $C_1$  and  $C_2$  are  $i_1$  and  $i_2$  respectively and voltages developed across  $C_1$ ,  $C_2$  are  $V_{C1}$  and  $V_{C2}$  respectively.



(a)

Capacitors in Parallel

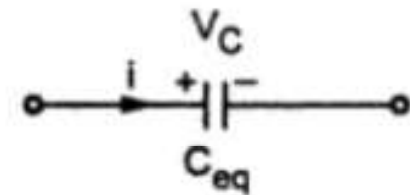

(b)

For capacitor we have,  $i_1 = C_1 \frac{dV_{C1}}{dt}$ ,  $i_2 = C_2 \frac{dV_{C2}}{dt}$ , while  $i = C_{eq} \frac{dV_C}{dt}$

# Capacitors in parallel

For parallel combination,

$$V_{C1} = V_{C2} = V_C \quad \text{and}$$

$$i = i_1 + i_2$$

$$C_{eq} \frac{dV_C}{dt} = C_1 \frac{dV_{C1}}{dt} + C_2 \frac{dV_{C2}}{dt}$$

$$\therefore C_{eq} \frac{dV_C}{dt} = (C_1 + C_2) \frac{dV_C}{dt}$$

$$\therefore C_{eq} = C_1 + C_2$$

That means, equivalent capacitance of the parallel combination of the capacitances is the sum of the individual capacitances connected in series.


For n capacitors in parallel,

$\therefore$

$$C_{eq} = C_1 + C_2 + \dots + C_n$$


# Example 8

Find the equivalent capacitance

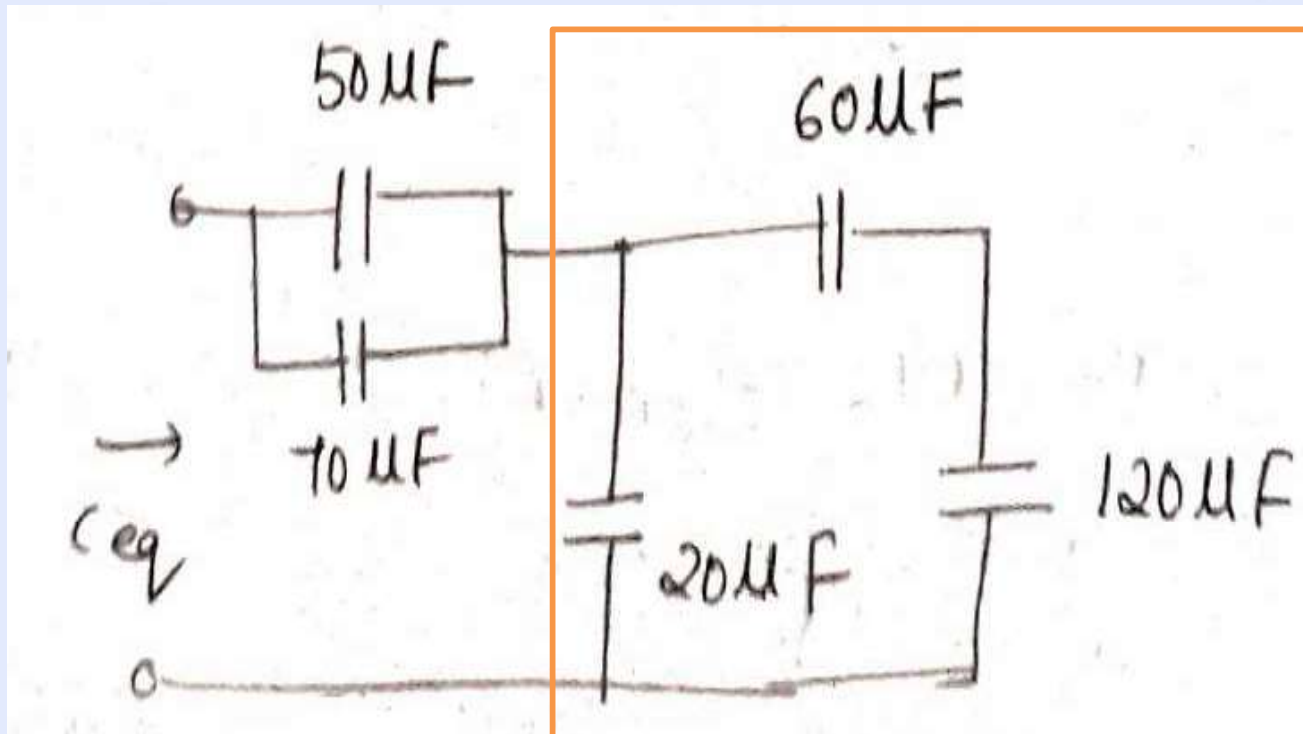


# Example 8

Find the equivalent capacitance

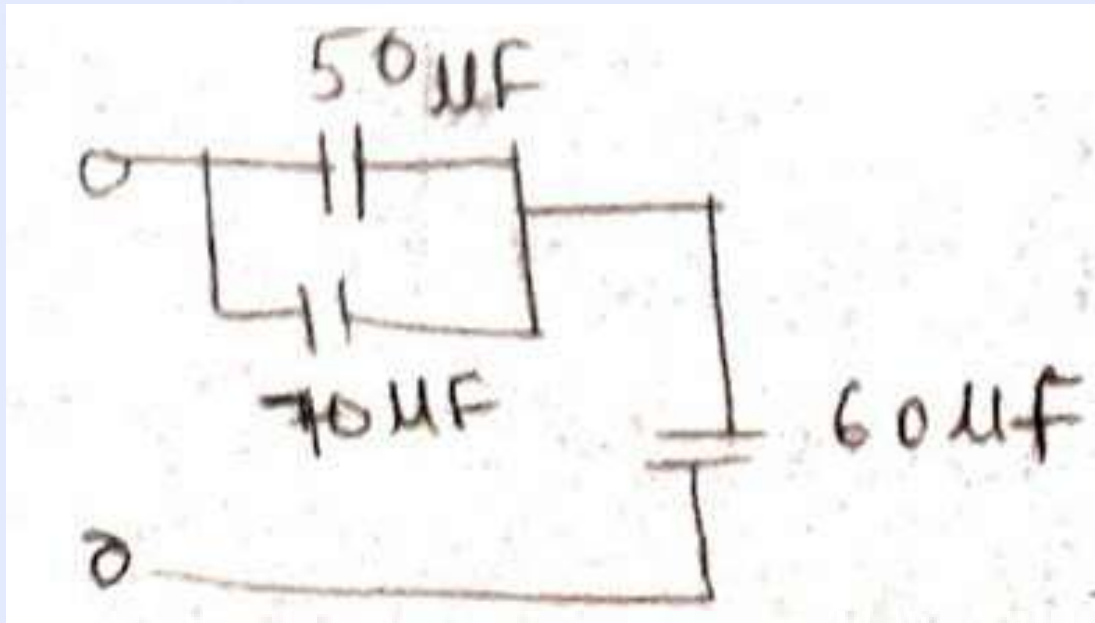

# Example 8

Find the equivalent capacitance

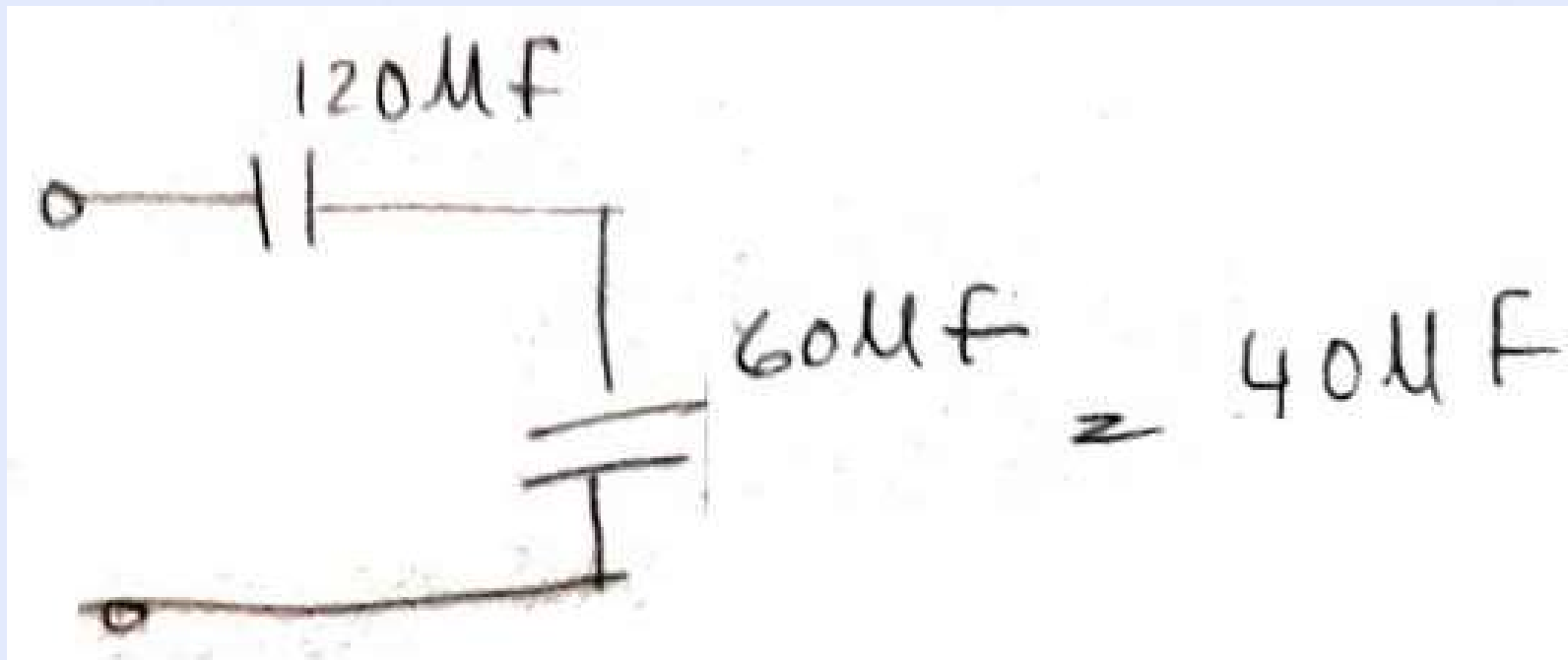



# Example 9

Calculate the combined capacitance in micro-Farads ( $\mu\text{F}$ ) of the following capacitors when they are connected together in a parallel combination:

- a) two capacitors each with a capacitance of  $47\text{nF}$
- b) one capacitor of  $470\text{nF}$  connected in parallel to a capacitor of  $1\mu\text{F}$

Solution:

a) Total Capacitance,

$$C_T = C_1 + C_2 = 47\text{nF} + 47\text{nF} = 94\text{nF} \text{ or } 0.094\mu\text{F}$$

b) Total Capacitance,

$$C_T = C_1 + C_2 = 470\text{nF} + 1\mu\text{F}$$

$$\text{therefore, } C_T = 470\text{nF} + 1000\text{nF} = 1470\text{nF} \text{ or } 1.47\mu\text{F}$$

# Example 10

Find the overall capacitance and the individual rms voltage drops across the following sets of two capacitors in **series** when connected to a 12V AC supply.

- a) two capacitors each with a capacitance of 47nF
- b) one capacitor of 470nF connected in series to a capacitor of 1 $\mu$ F

# Example 10

a) Total Equal Capacitance,

$$C_T = \frac{C_1 \times C_2}{C_1 + C_2} = \frac{47\text{nF} \times 47\text{nF}}{47\text{nF} + 47\text{nF}} = 23.5\text{nF}$$

Voltage drop across the two identical 47nF capacitors,

$$V_{C1} = \frac{C_T}{C_1} \times V_T = \frac{23.5\text{nF}}{47\text{nF}} \times 12\text{V} = 6\text{volts}$$

$$V_{C2} = \frac{C_T}{C_2} \times V_T = \frac{23.5\text{nF}}{47\text{nF}} \times 12\text{V} = 6\text{volts}$$

# Example 10

b) Total Unequal Capacitance,

$$C_T = \frac{C_1 \times C_2}{C_1 + C_2} = \frac{470\text{nF} \times 1\mu\text{F}}{470\text{nF} + 1\mu\text{F}} = 320\text{nF}$$


Voltage drop across the two non-identical Capacitors:  $C_1 = 470\text{nF}$  and  $C_2 = 1\mu\text{F}$ .

$$V_{C1} = \frac{C_T}{C_1} \times V_T = \frac{320\text{nF}}{470\text{nF}} \times 12 = 8.16\text{volts}$$

$$V_{C2} = \frac{C_T}{C_2} \times V_T = \frac{320\text{nF}}{1\mu\text{F}} \times 12 = 3.84\text{volts}$$
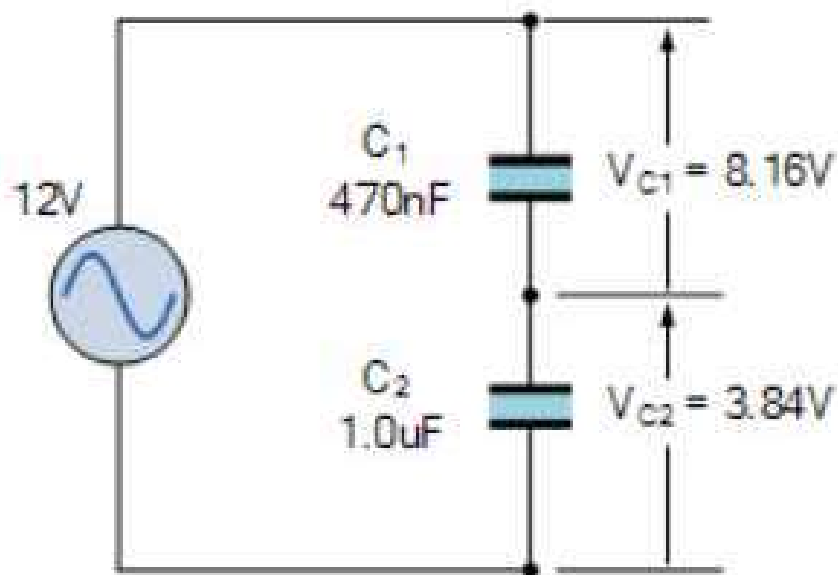
# Example 10

The difference in voltage allows the capacitors to maintain the same amount of charge,  $Q$  on the plates of each capacitors as shown.




$$Q_{C1} = V_{C1} \times C_1 = 8.16V \times 470nF = 3.84\mu C$$

$$Q_{C2} = V_{C2} \times C_2 = 3.84V \times 1\mu F = 3.84\mu C$$
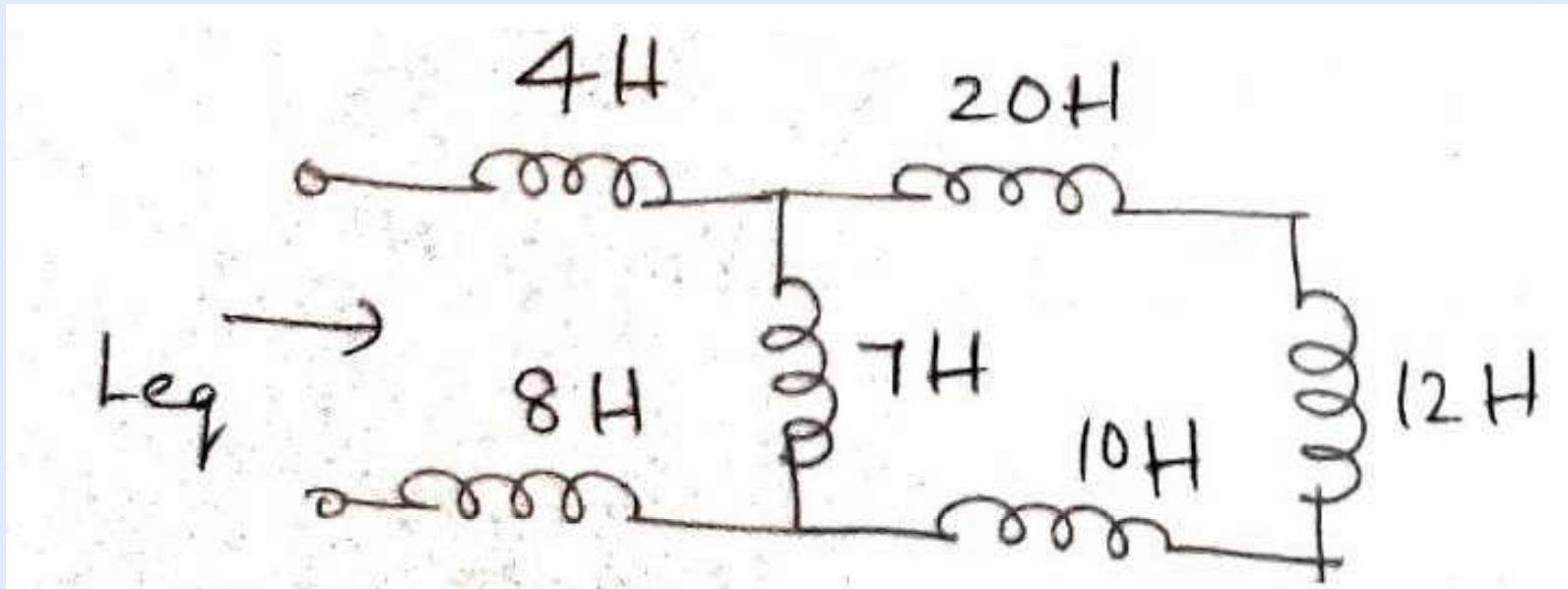
# Example 11

Find the equivalent Inductance of the given circuit



$$L_{eq} = 18 H$$

# Example 12


Three inductors of 60mH, 120mH and 75mH respectively, are connected together in a parallel combination with no mutual inductance between them. Calculate the total inductance of the parallel combination in millihenries.

**Solution:**

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$\therefore L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}} = \frac{1}{\frac{1}{60\text{mH}} + \frac{1}{120\text{mH}} + \frac{1}{75\text{mH}}}$$

$$L_T = \frac{1}{38.333} = 26\text{mH}$$

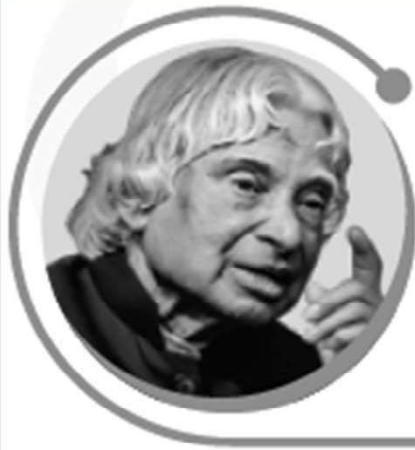

“ Amrita Vishwa Vidyapeetham has a major role to play in transforming our society into a knowledge society through its unique value-added education system.

*Dr. A.P.J. Abdul Kalam*  
Former President of India

”

# THANK YOU